



Electronics and digital logic

Yuning You

School of Science and Engineering
The Chinese University of Hong Kong, Shenzhen


Recap: Microcontroller chip in practice

Chip diagram

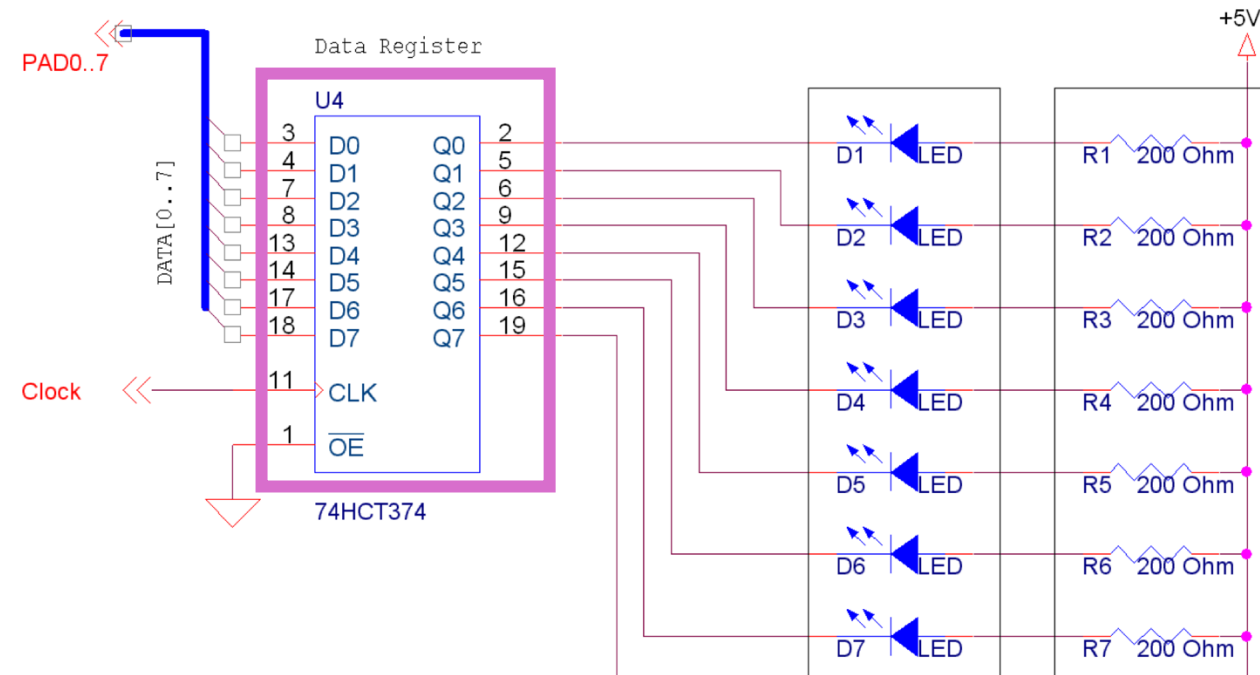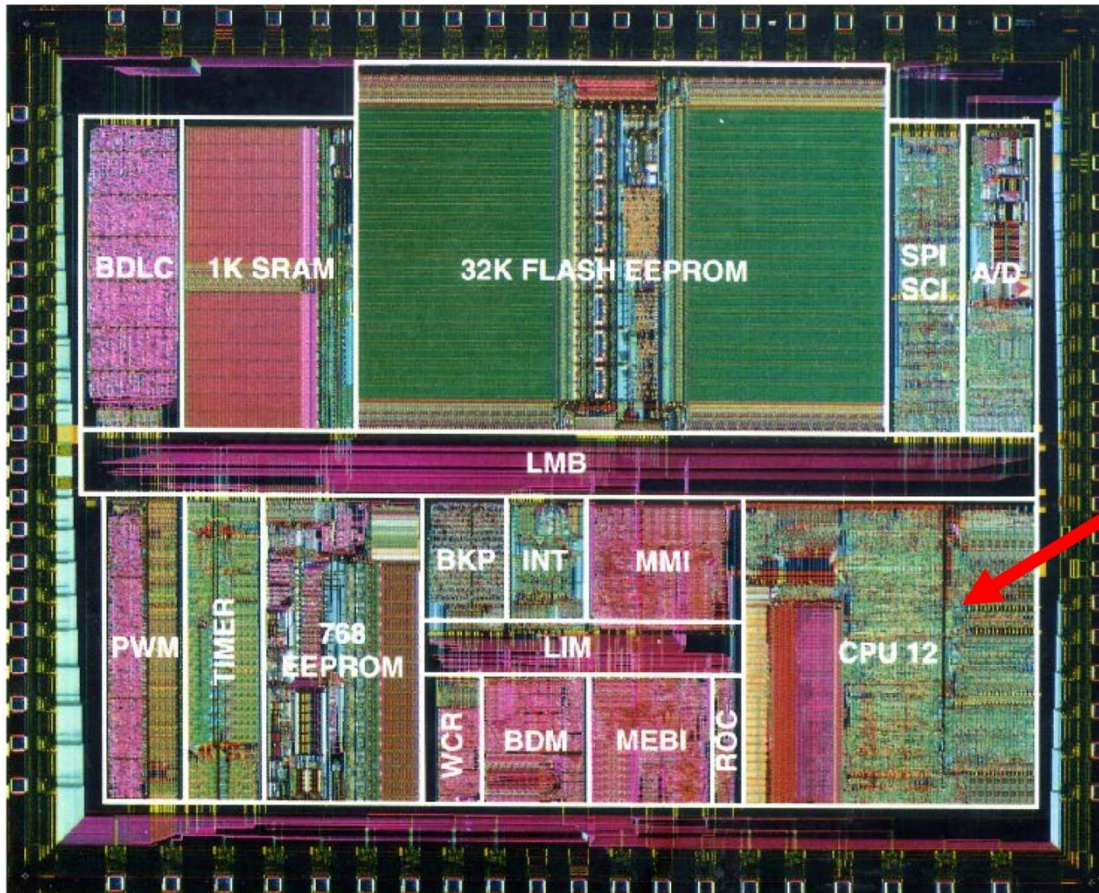


Fundamental unit: Electronic circuit (transistor)

Circuit diagram

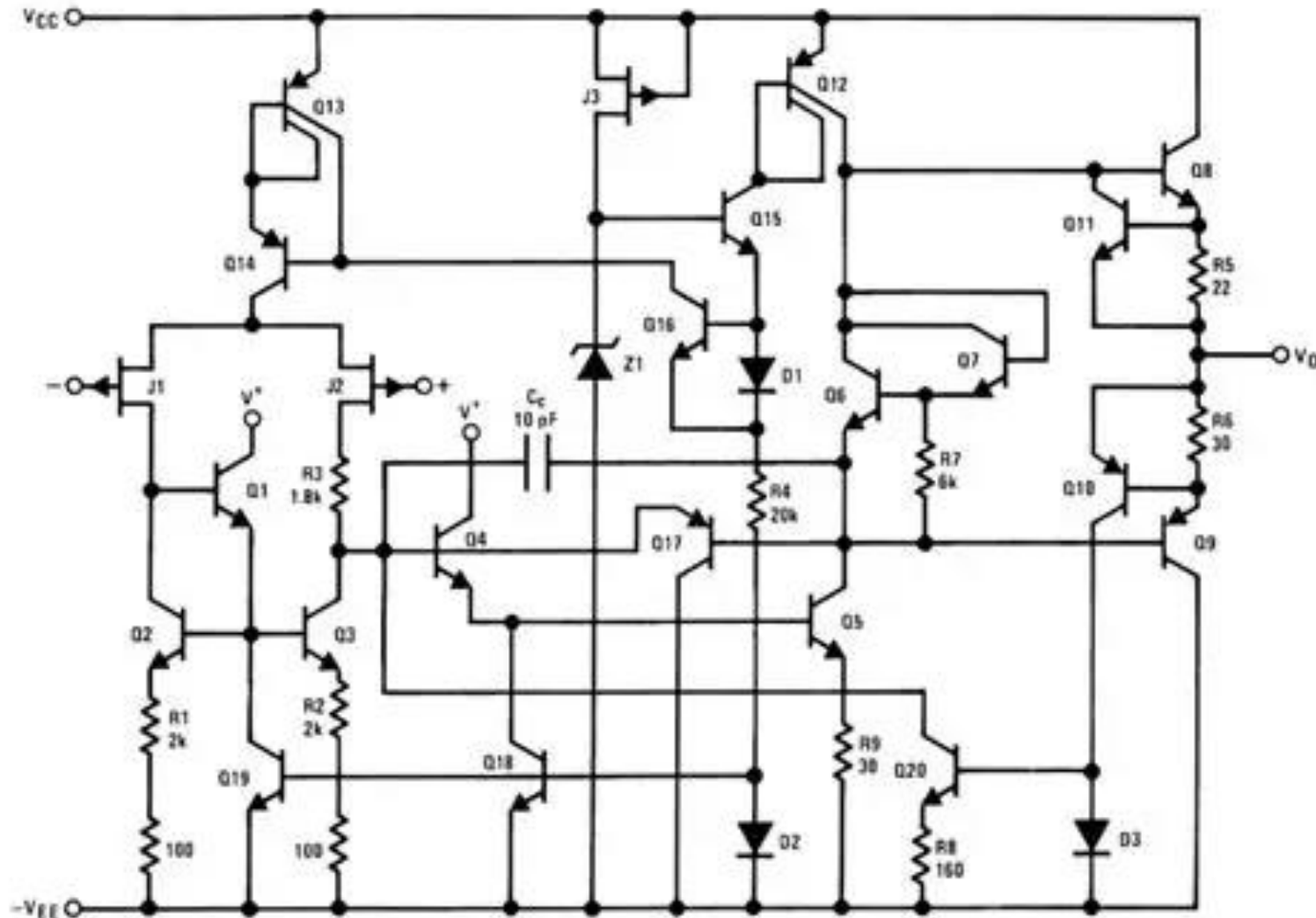


Digital logic

Buffer

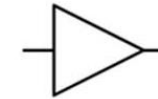

Input	Output
0	0
1	1

AND

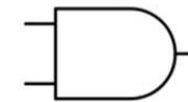

A	B	Output
0	0	0
1	0	0
0	1	0
1	1	1

OR




A	B	Output
0	0	0
1	0	1
0	1	1
1	1	1

XOR




A	B	Output
0	0	0
1	0	1
0	1	1
1	1	0


Circuit schematics

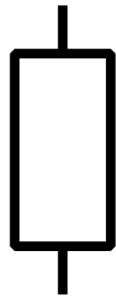


Block
element

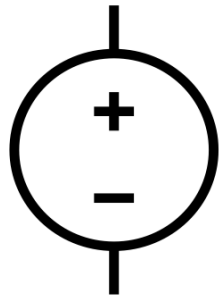



Voltage
source

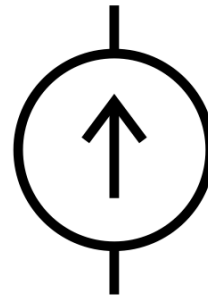


Current
source

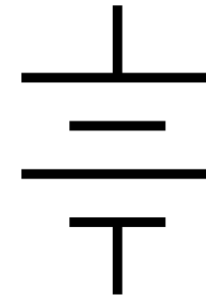





Battery

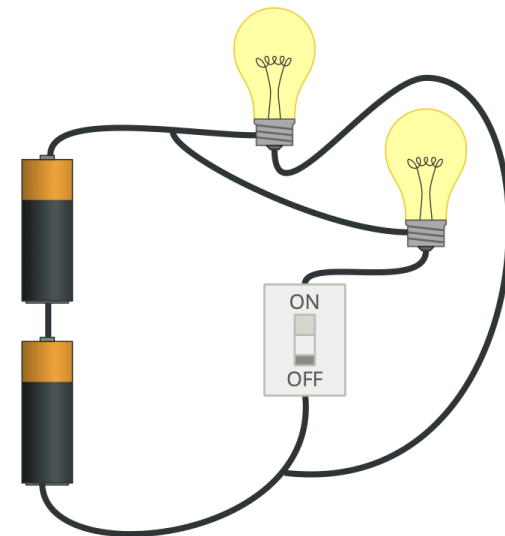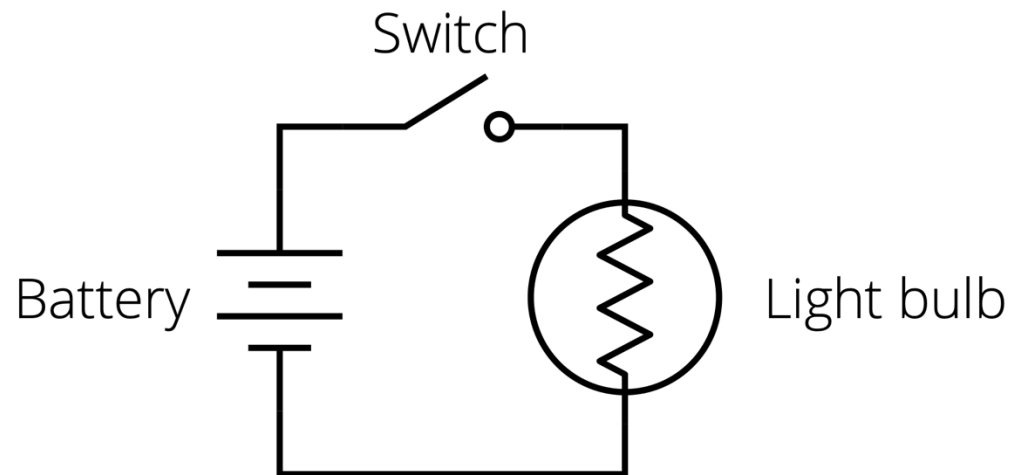




Congruent schematics

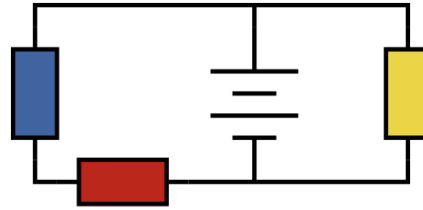

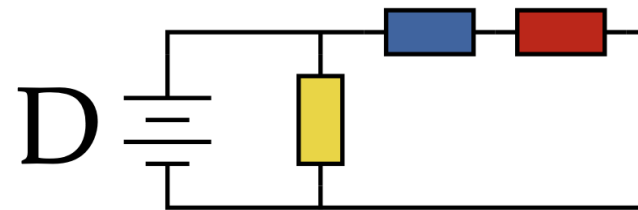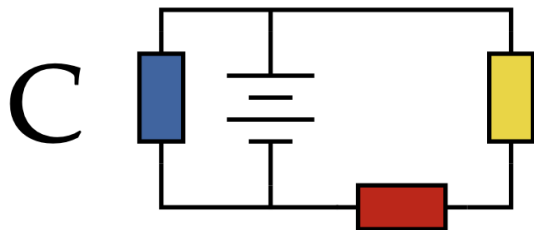
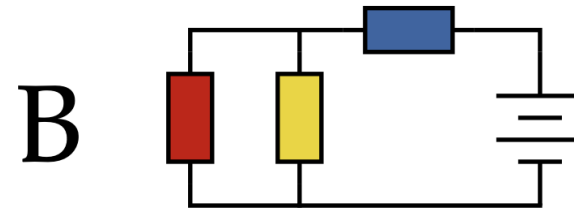
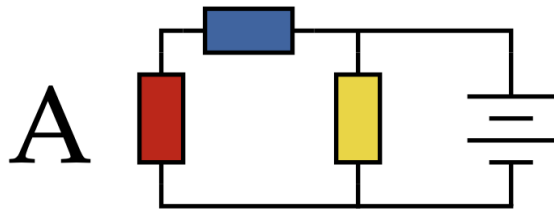
Which of the circuits below are congruent with the circuit above?






Current and voltage have signs

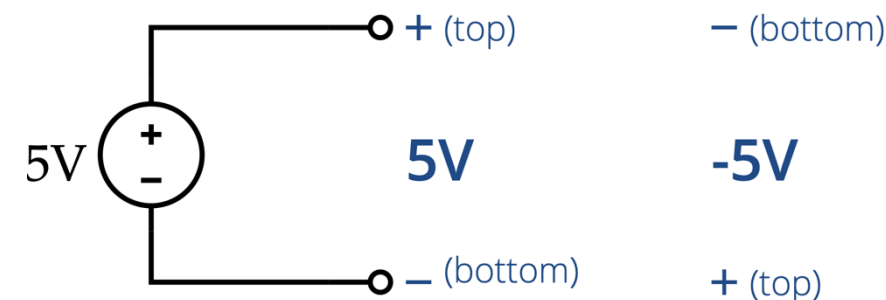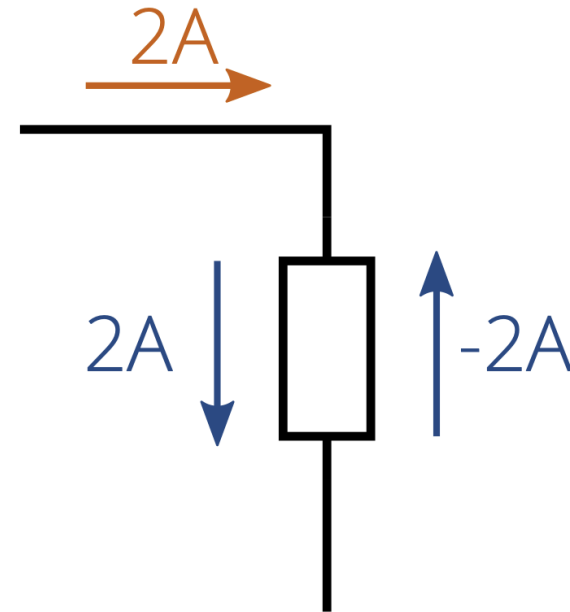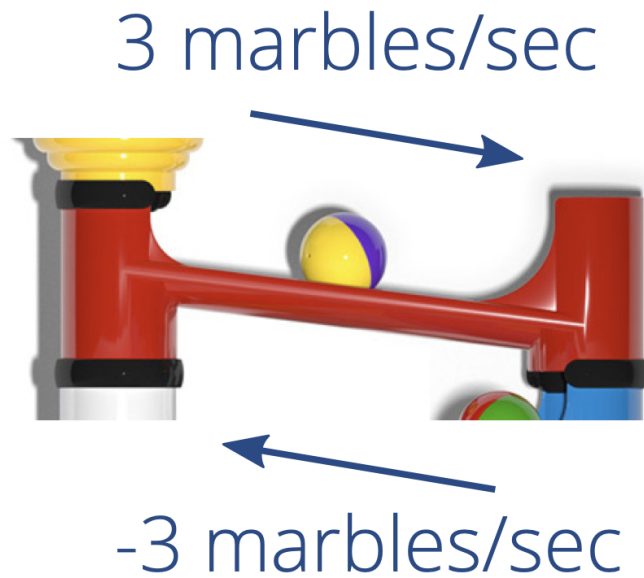


Kirchoff's current law

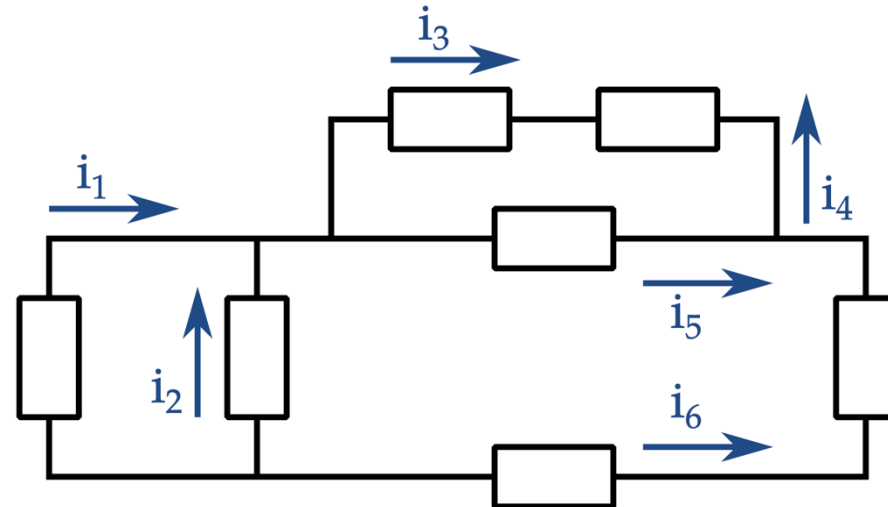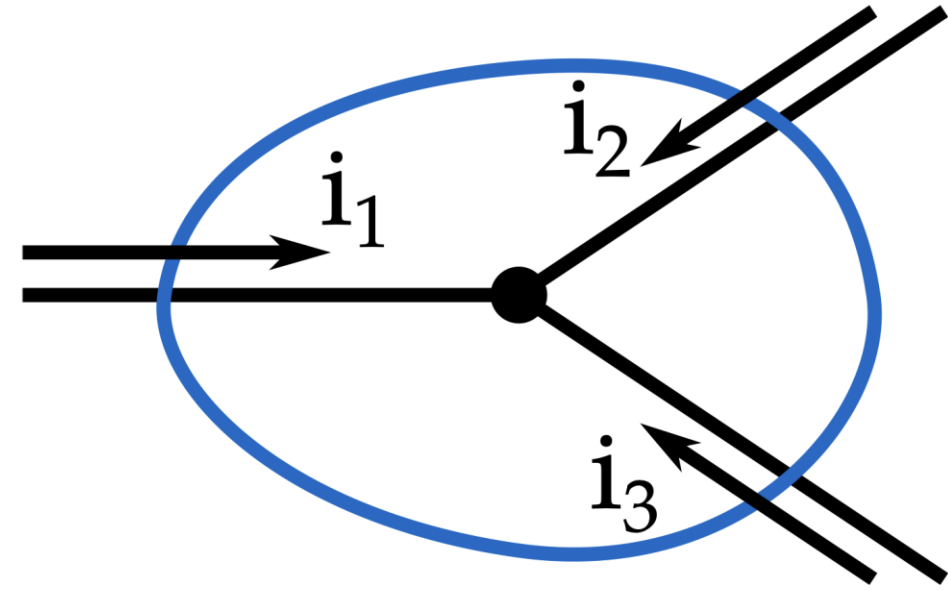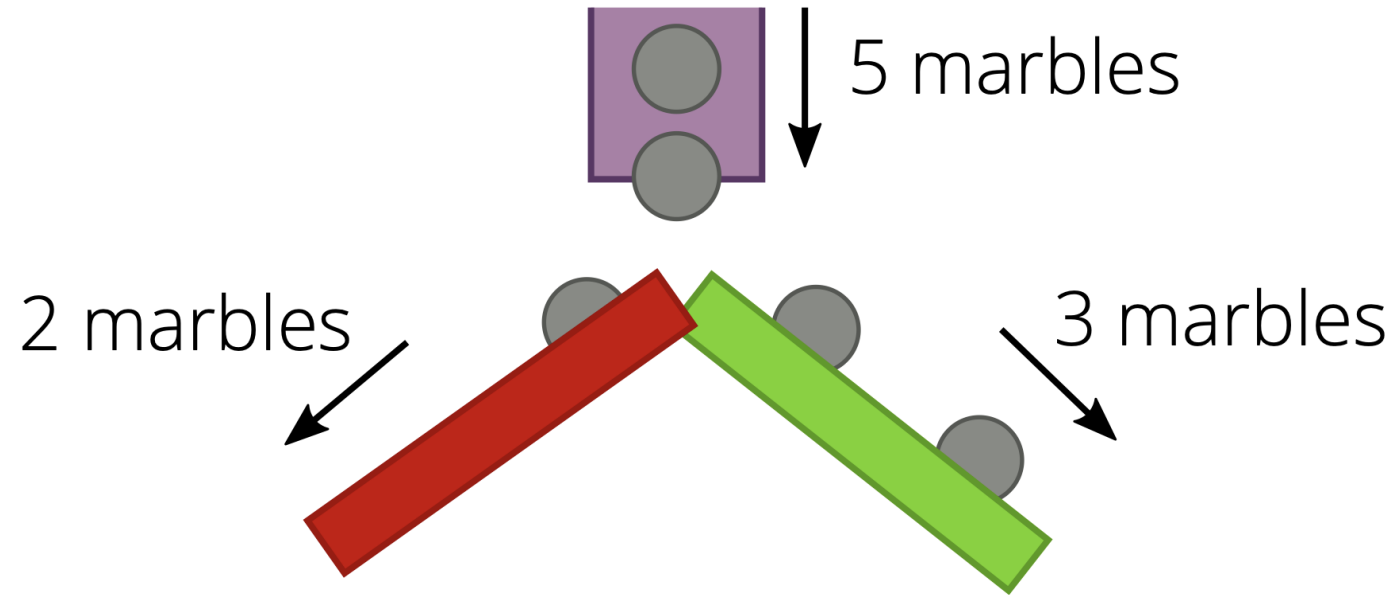

Kirchoff's voltage law

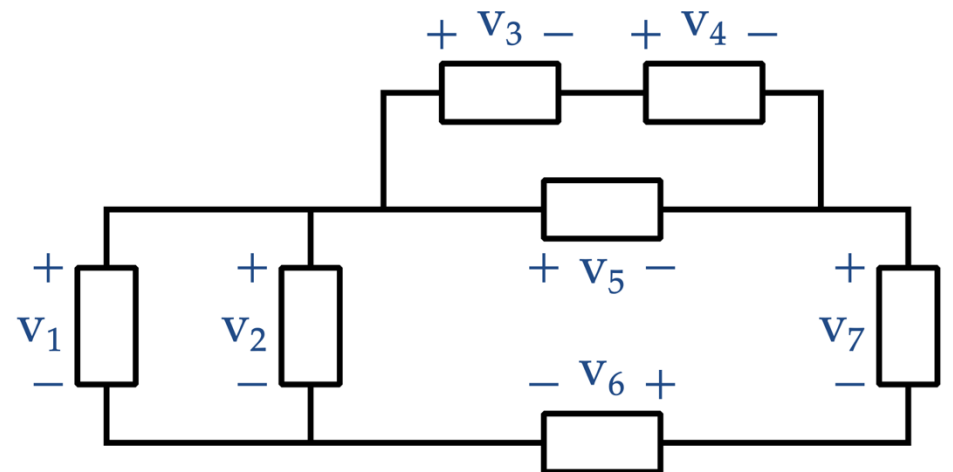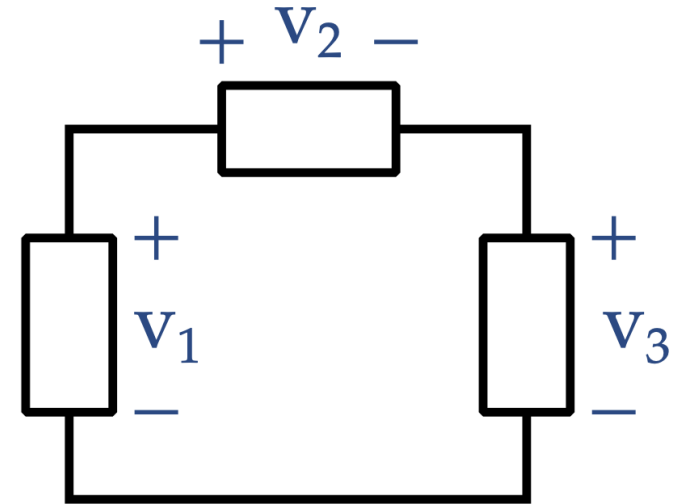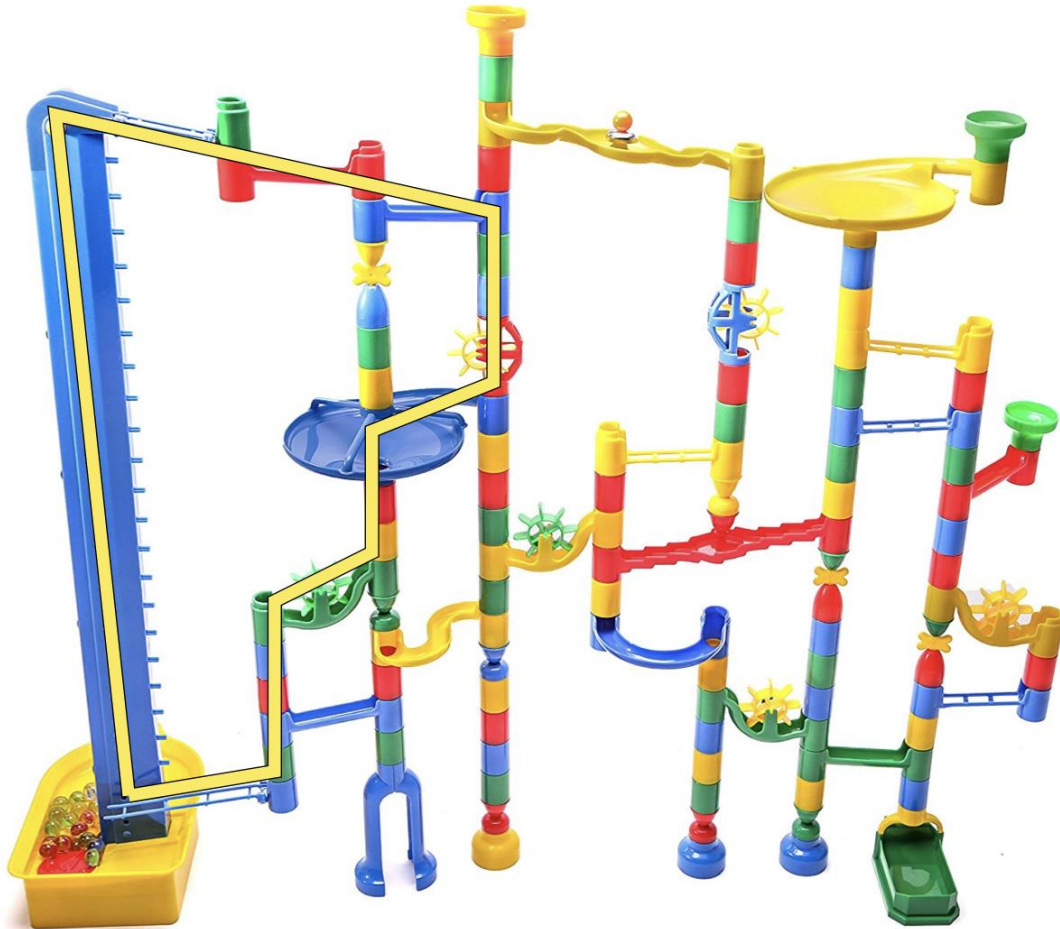


Find the voltage V_2 and current I_2

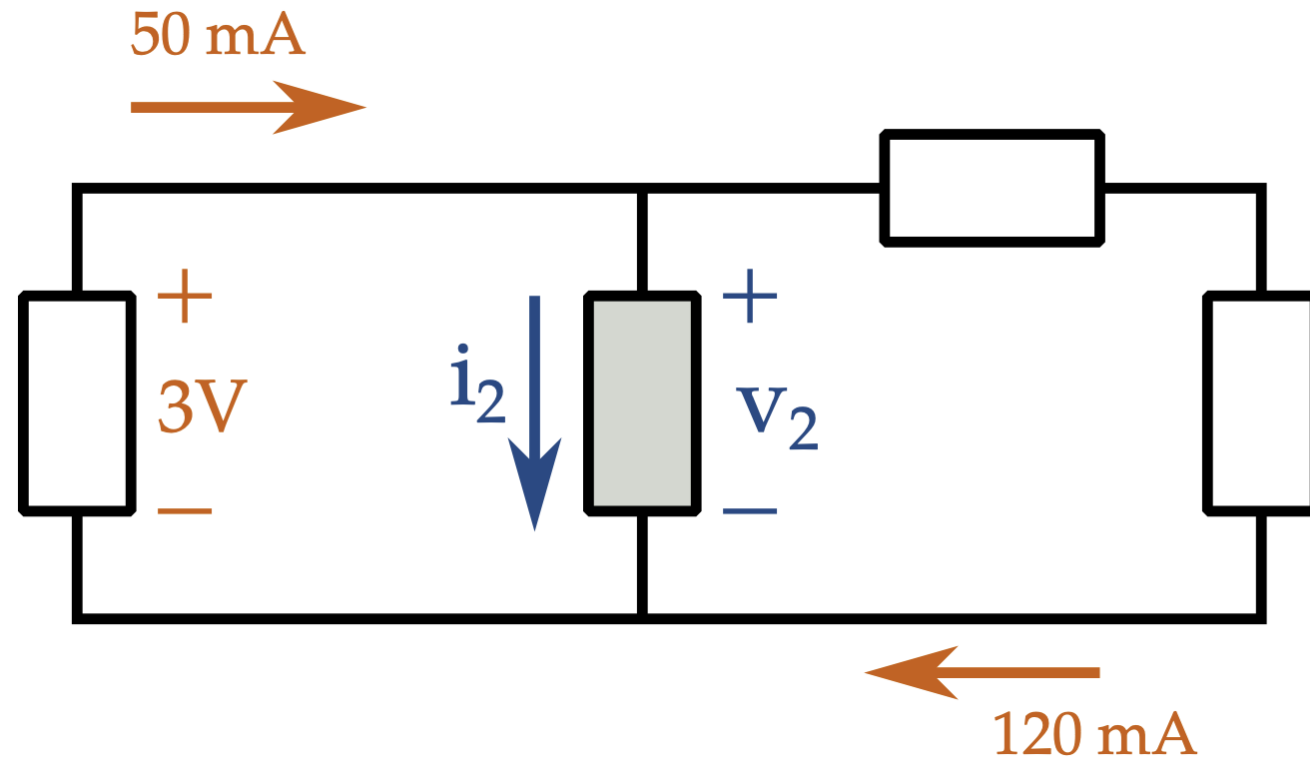

Is the gray element absorbing or supplying electrical energy?

Joule's law of electric power

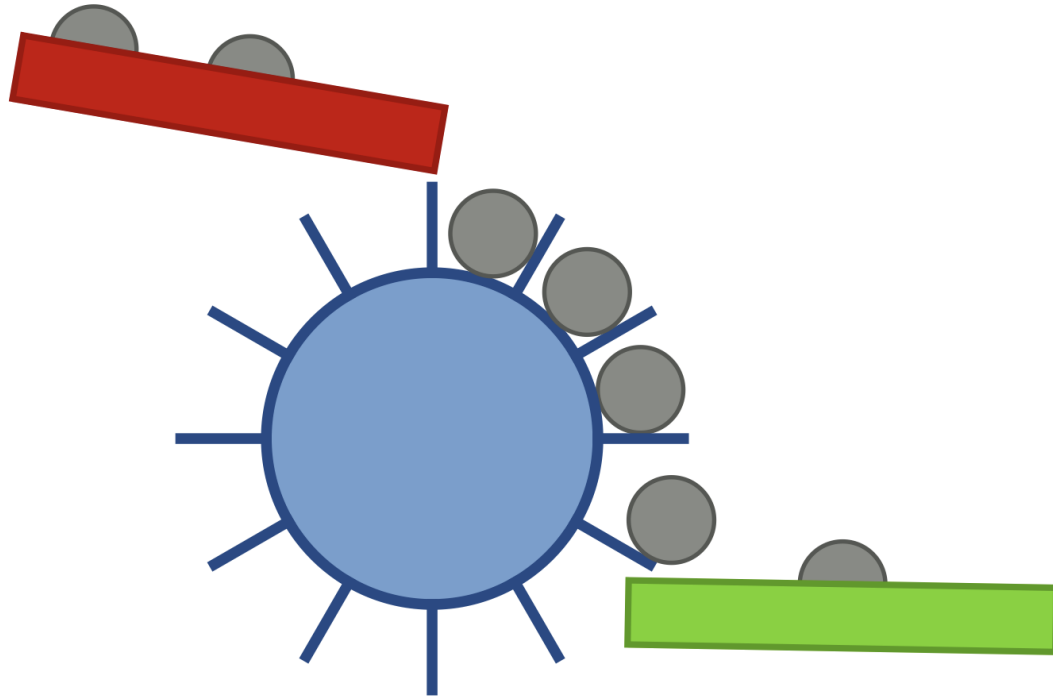


Power (P) = Voltage (V) × Current (I)
at the unit of Watt
(abbreviated as W)

How much power does a light bulb use,
if it is connected to 120V and draws 0.5 A?

Resistor and Ohm's law


Marble-track resistor

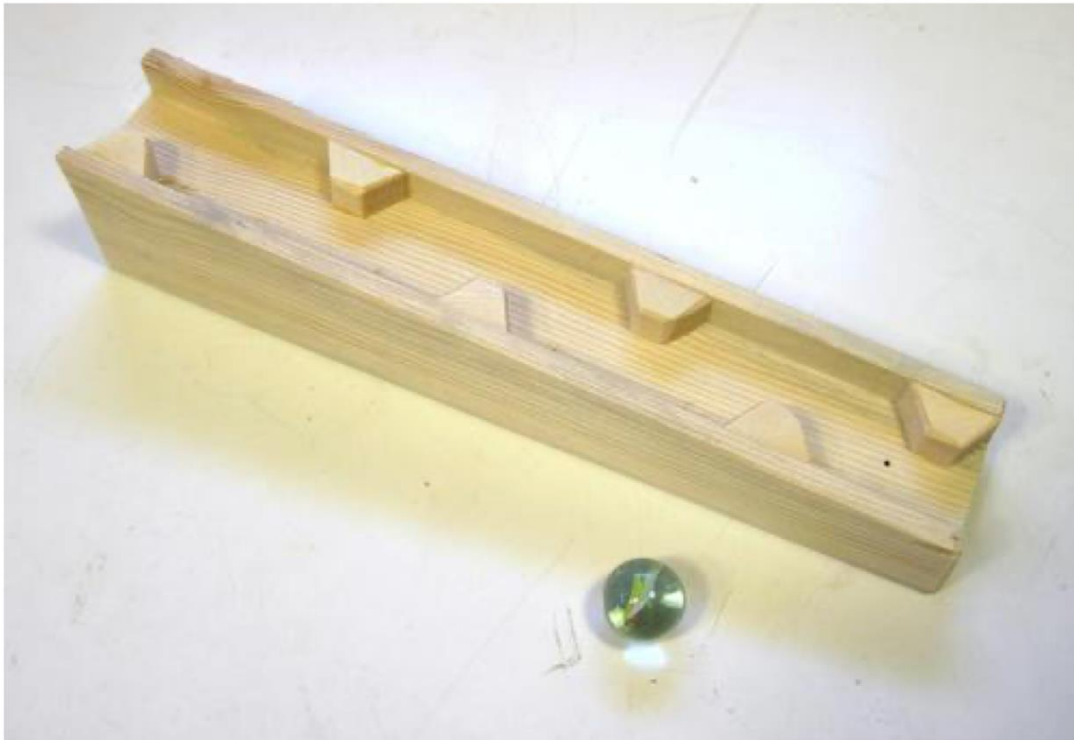


Ohm's law:

$$I = V / R$$


Current = Voltage / Resistance

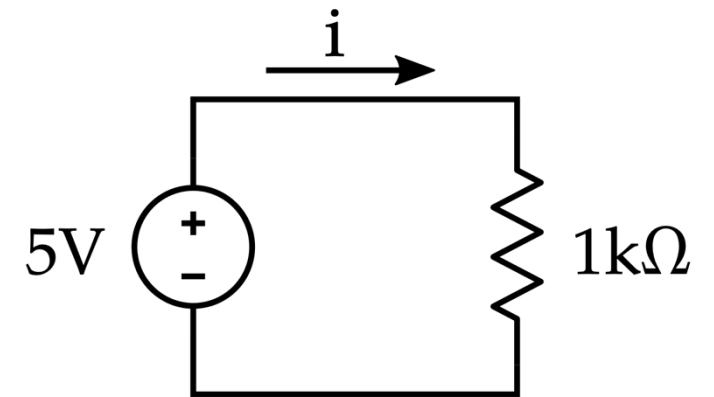

Series/parallel resistors

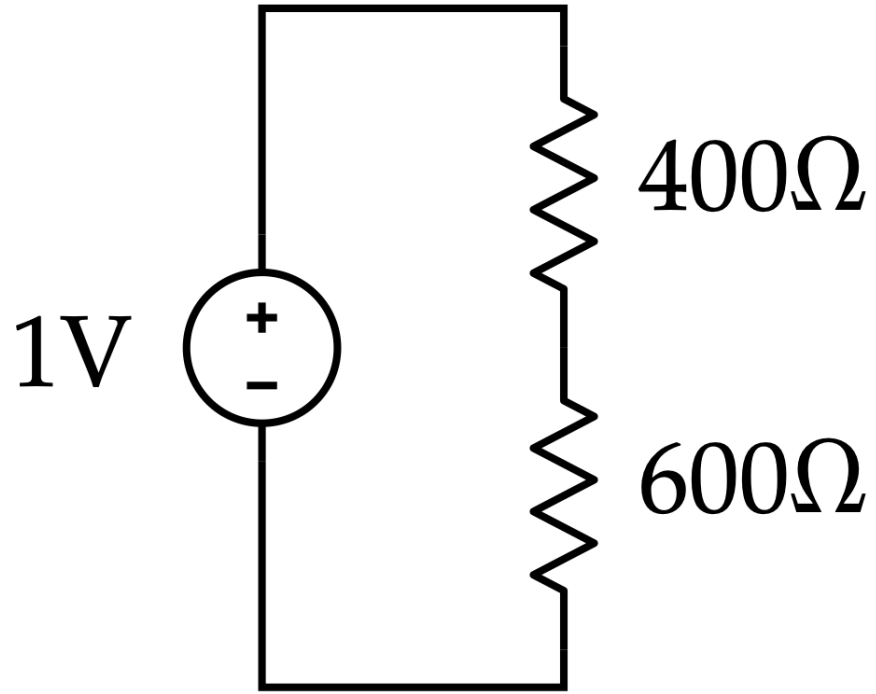


$$R_{eff} = R_1 + R_2$$

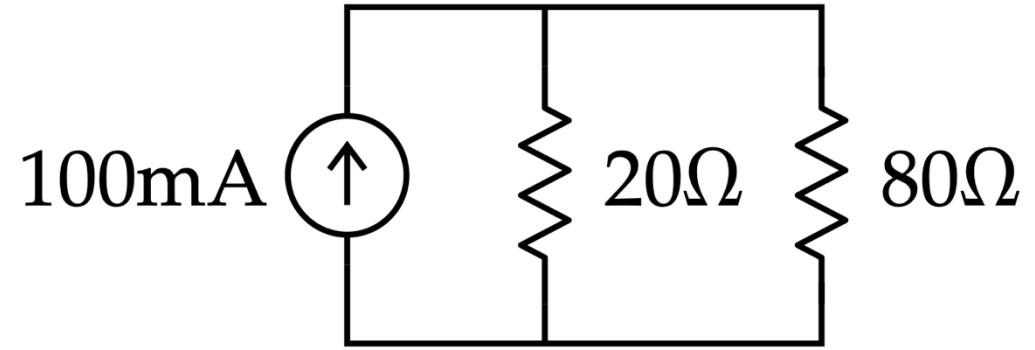



$$\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eff} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$


Practice

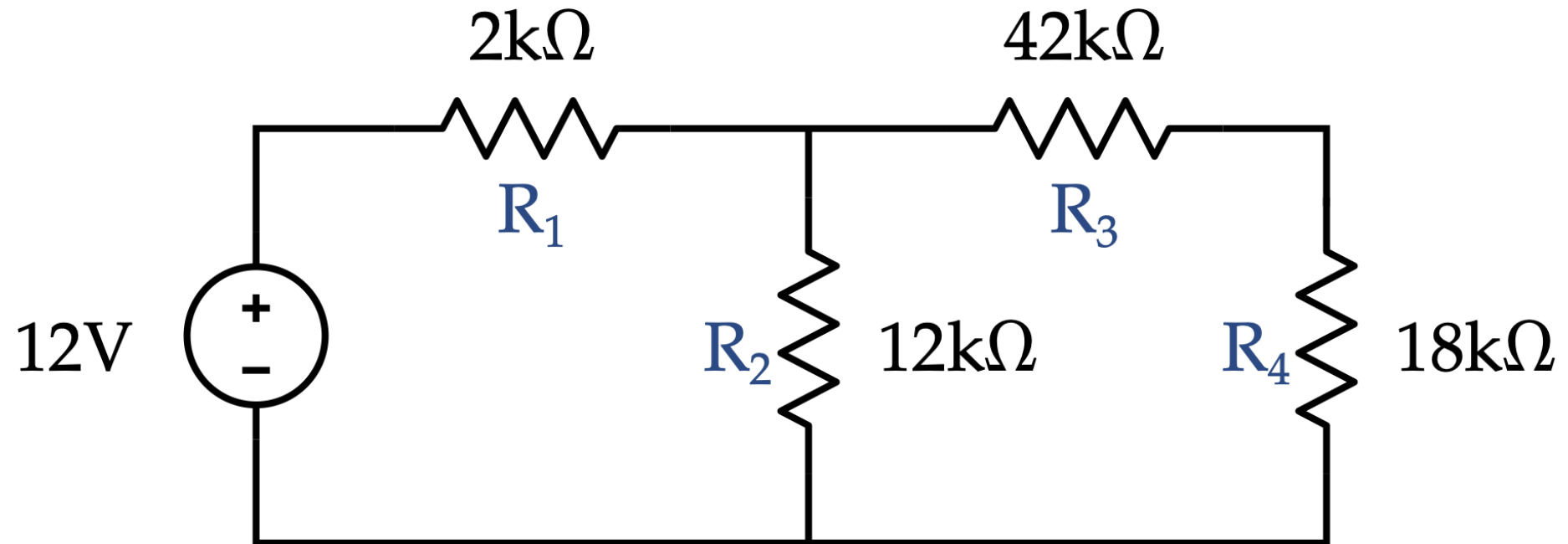

Diode: One-way valves for current

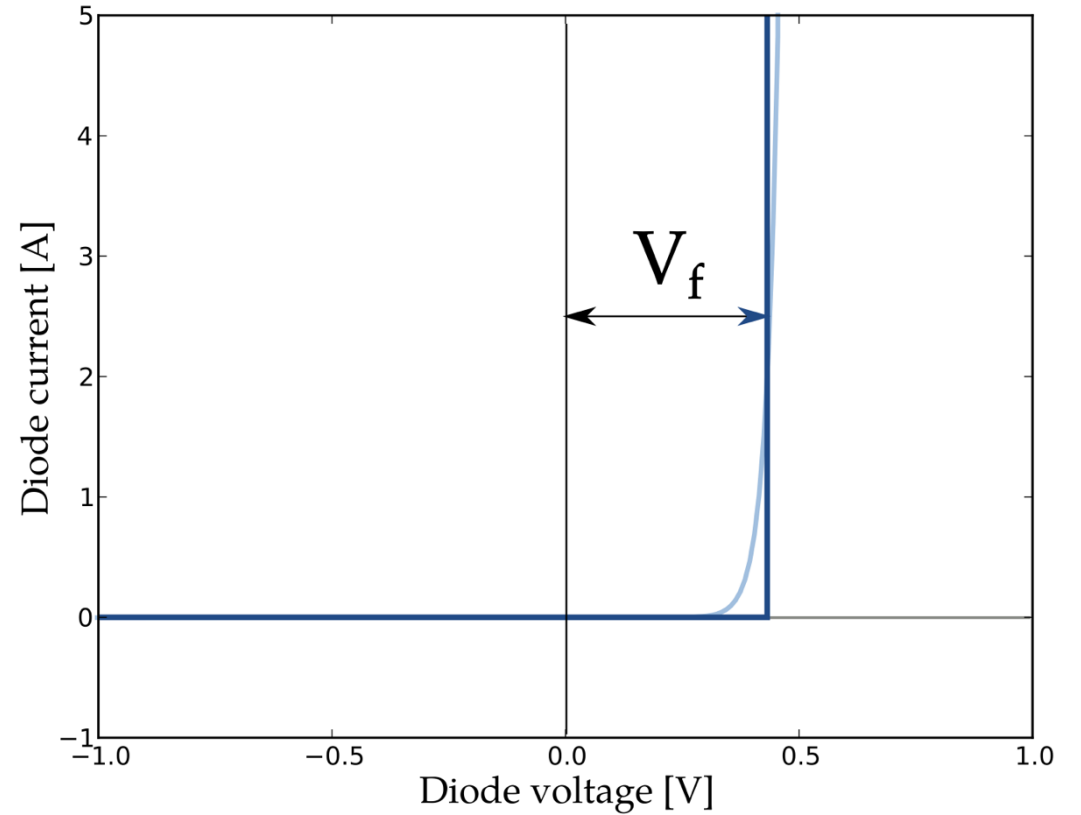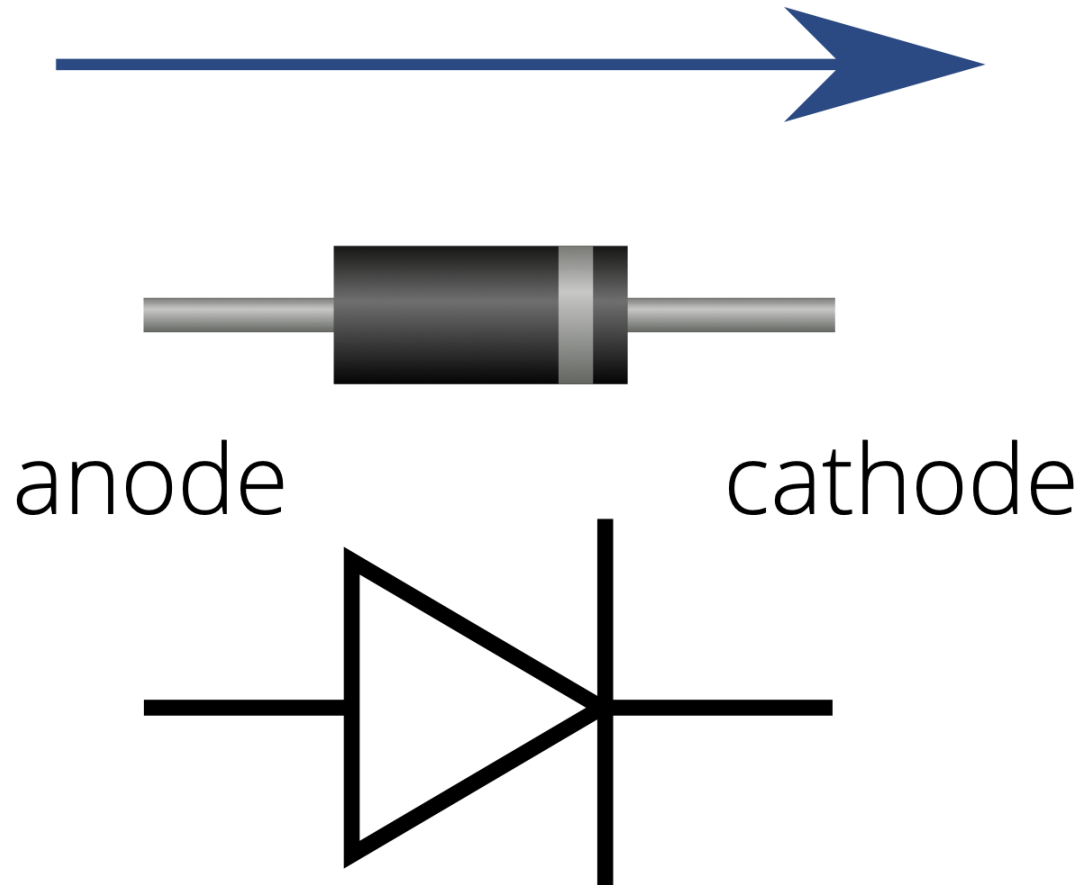



Diode practice

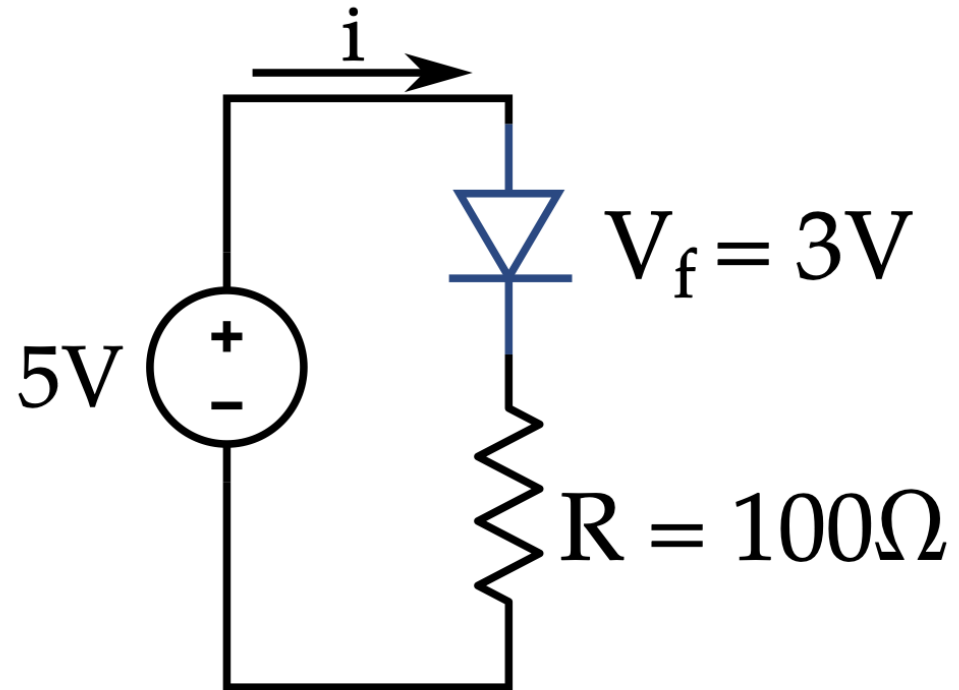


- What is the current through the diode?
- What is the voltage at the resistor?

Transistor

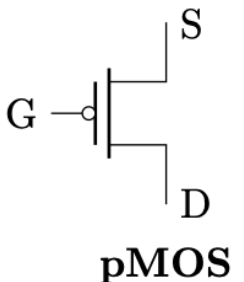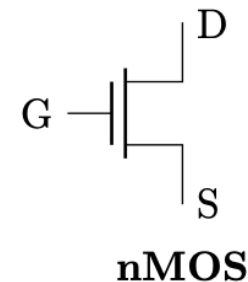
- A transistor is an electronic device that is used to allow one electrical signal to control another electrical signal
- Metal–oxide–semiconductor field-effect transistor (MOS/MOSFET)
- MOSFETs come in two types: the n-channel MOSFET (nMOS) and the p-channel MOSFET (pMOS)
- Three terminals: the gate, drain and source




Ideal MOS transistor switch

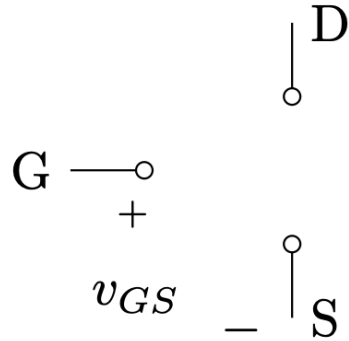


nMOS off: $v_{GS} < V_{th}$

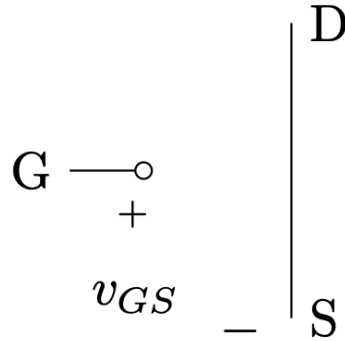


nMOS on: $v_{GS} > V_{th}$

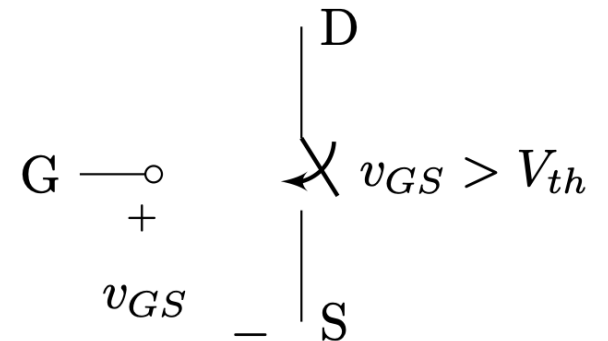


nMOS model

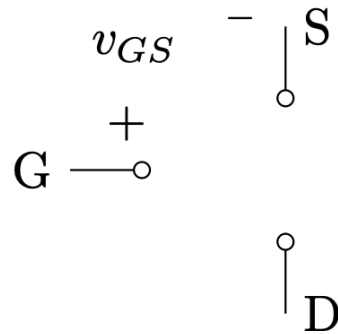

pMOS off: $v_{GS} > -V_{th}$

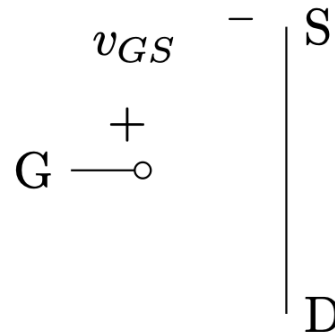


pMOS on: $v_{GS} < -V_{th}$

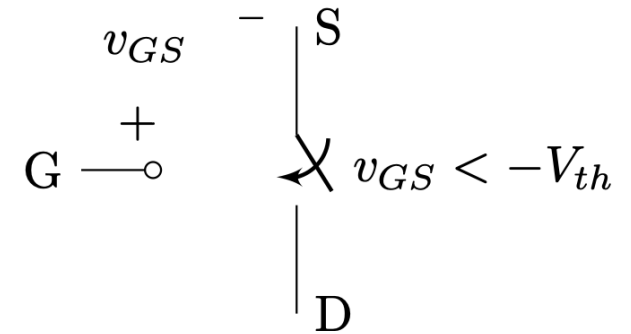


pMOS model


Modeling internal resistance

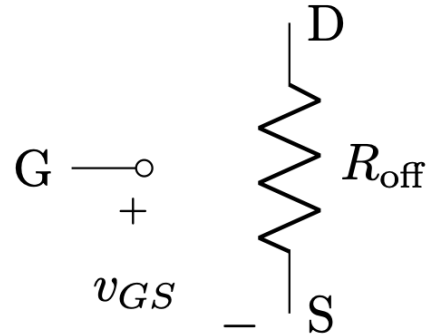


nMOS off: $v_{GS} < V_{th}$

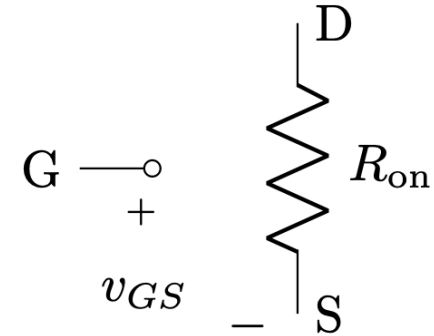

nMOS on: $v_{GS} > V_{th}$

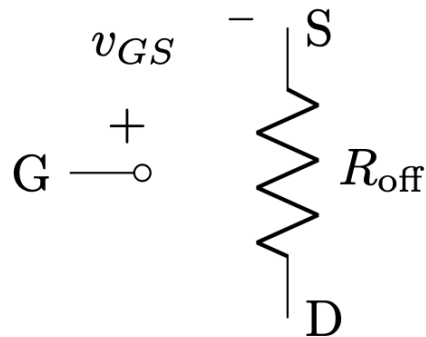


pMOS off: $v_{GS} > -V_{th}$

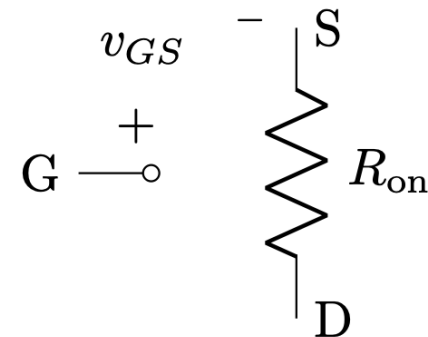

pMOS on: $v_{GS} < -V_{th}$


Practice

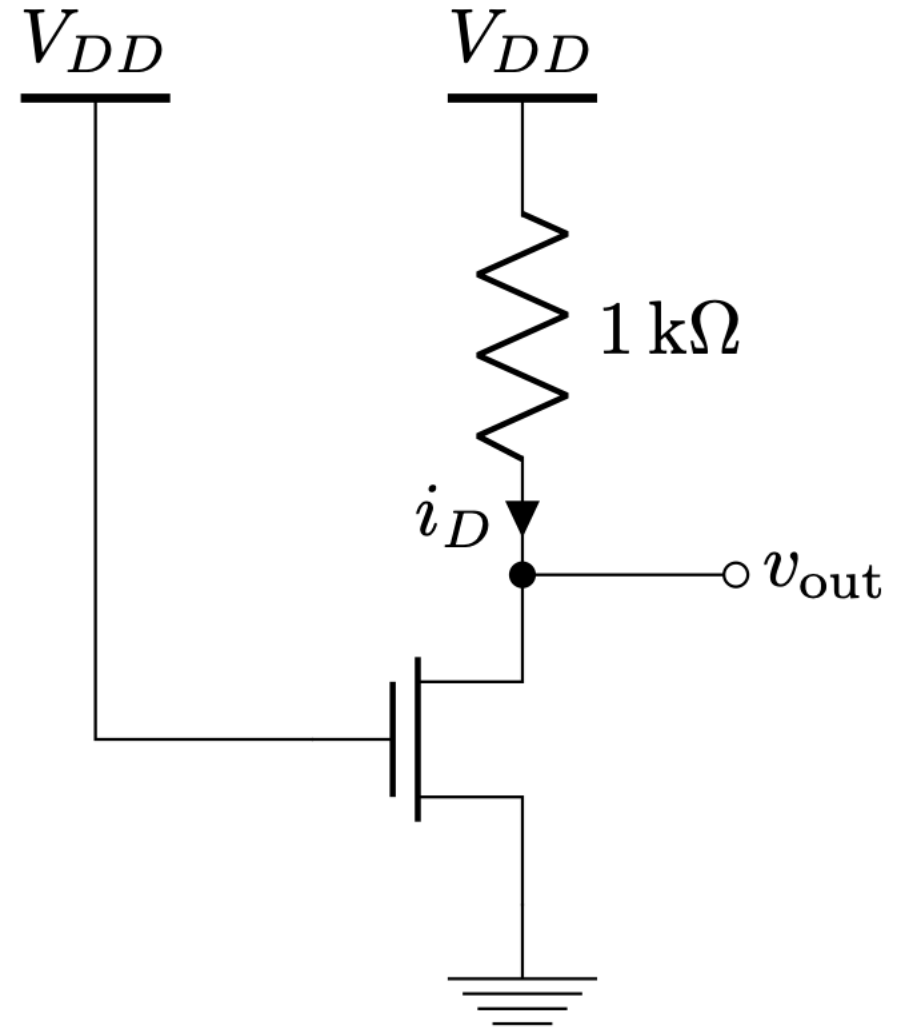- $V_{DD}=5V$, $V_{th}=1V$ for transistors
- What is v_{out} ?
- What is i_D ?




Practice

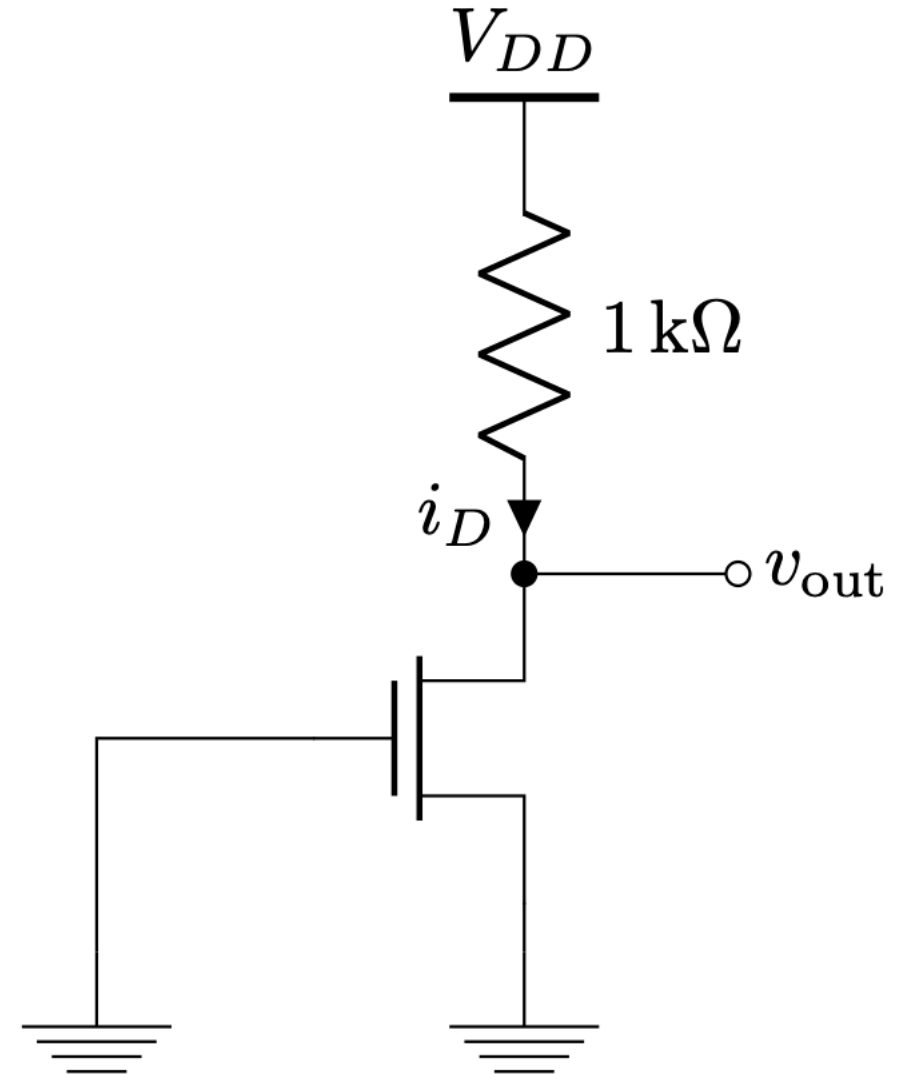- $V_{DD}=5V$, $V_{th}=1V$ for transistors
- What is v_{out} ?
- What is i_D ?



Practice

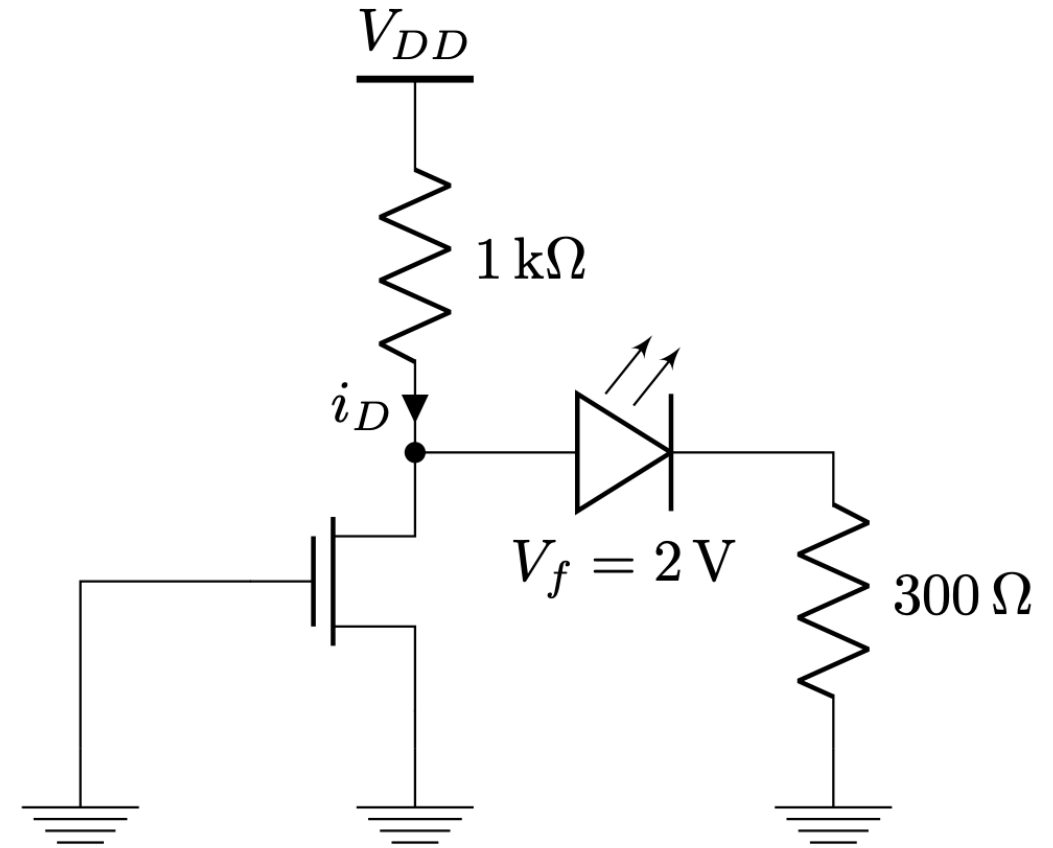
- $V_{DD}=5V$, $V_{th}=1V$ for transistors
- What is the current through the LED?



Recap: Running LEDs

- <https://wokwi.com/projects/447390165530456065>
- Can you light up one more LED only when the last two running LEDs are on?

```
1 // 4-bit binary counter using LEDs (each LED toggles at different rates)
2
3 int ledPin[] = {13, 12, 11, 10}; // LED pins: MSB → LSB
4 int ledDelay[] = {8000, 4000, 2000, 1000}; // toggle interval (ms)
5 unsigned long lastChangeTime[4]; // store last toggle time of each LED
6 int ledState[4] = {LOW, LOW, LOW, LOW}; // store current state (LOW/HIGH)
7 unsigned long currTime; // current time variable
8
9 void setup() {
10   currTime = 0; // initialize timer
11   for (int i = 0; i < 4; i++) {
12     pinMode(ledPin[i], OUTPUT); // set pin as output
13     digitalWrite(ledPin[i], ledState[i]); // turn LED off initially
14     lastChangeTime[i] = millis(); // record initial time
15   }
16   pinMode(8, OUTPUT);
17   digitalWrite(8, LOW);
18 }
19
20 void loop() {
21   currTime = millis(); // get current time
22
23   for (int i = 0; i < 4; i++) { // check all LEDs
24     if (currTime - lastChangeTime[i] >= ledDelay[i]) {
25       // time to toggle the LED
26       ledState[i] = !ledState[i]; // flip LED state
27       digitalWrite(ledPin[i], ledState[i]); // apply new state
28       lastChangeTime[i] = currTime; // reset timer for that LED
29     }
30
31     if (ledState[0] == HIGH && ledState[1] == HIGH &&
32         ledState[2] == HIGH && ledState[3] == HIGH) {
33       digitalWrite(8, HIGH);
34     } else {
35       digitalWrite(8, LOW);
36     }
37   }
38 }
```

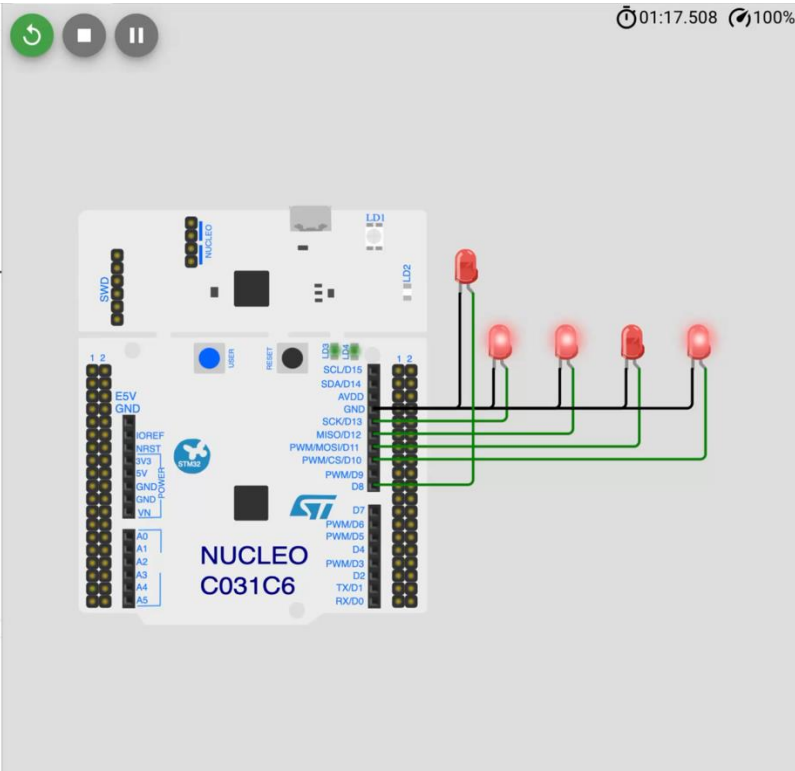


Virtual lab session: Running LEDs with digital logics

Virtual lab session: Running LEDs with digital logics


- Can you light up one more LED only when the all four running LEDs are on?

Recap: Fundamental unit: Electronic circuit (transistor)


Circuit diagram

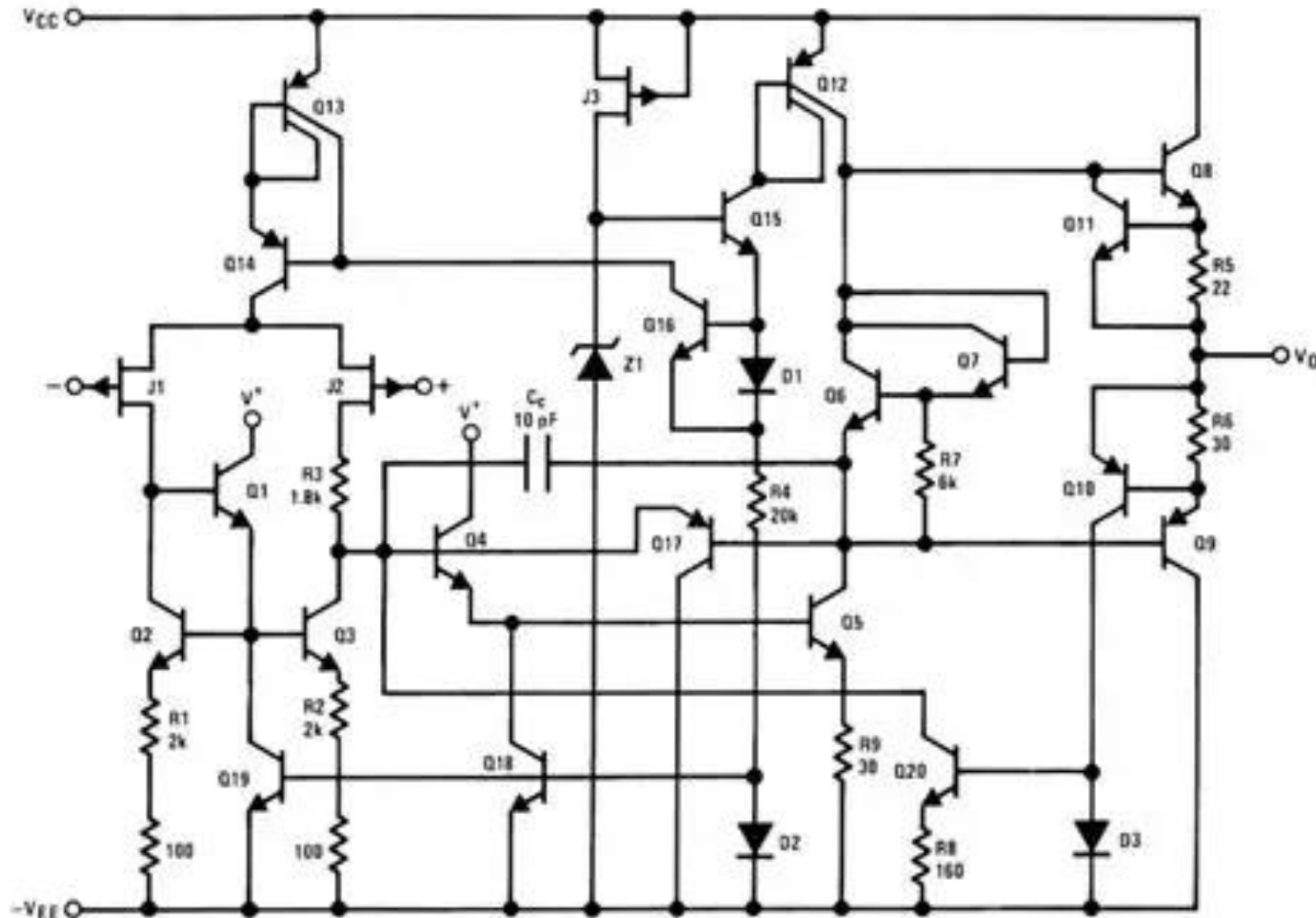


Digital logic

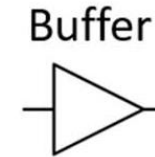


Input	Output
0	0
1	1

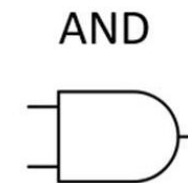

A	B	Output
0	0	0
1	0	0
0	1	0
1	1	1

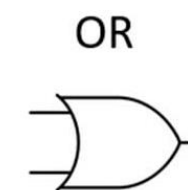

A	B	Output
0	0	0
1	0	1
0	1	1
1	1	1


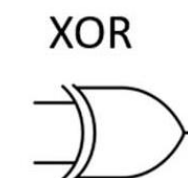


A	B	Output
0	0	0
1	0	1
0	1	1
1	1	0


Recap: Transistor

- A transistor is an electronic device that is used to allow one electrical signal to control another electrical signal
- Metal–oxide–semiconductor field-effect transistor (MOS/MOSFET)
- MOSFETs come in two types: the n-channel MOSFET (nMOS) and the p-channel MOSFET (pMOS)

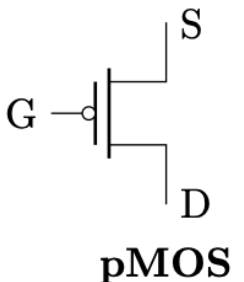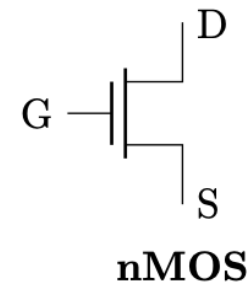
- Three terminals: the gate, drain and source




Recap: Ideal MOS transistor switch

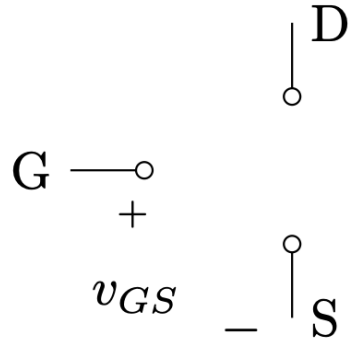


nMOS off: $v_{GS} < V_{th}$

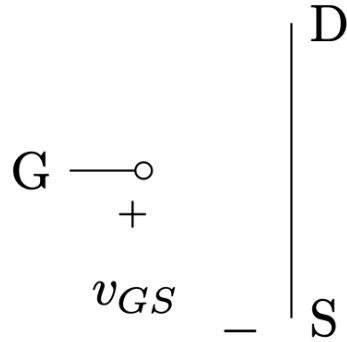


nMOS on: $v_{GS} > V_{th}$

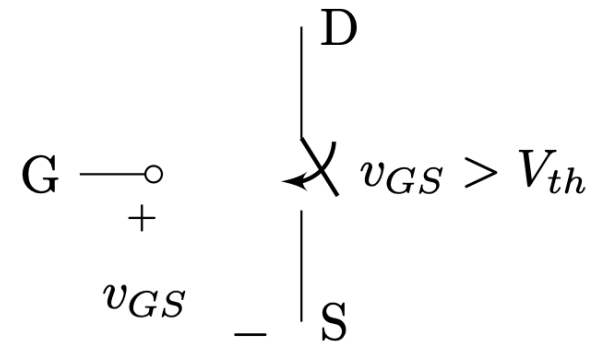


nMOS model

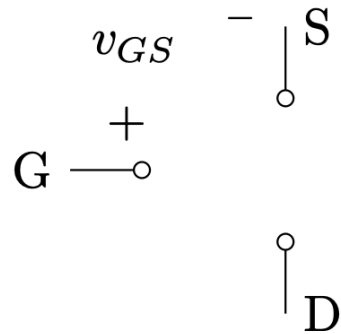

pMOS off: $v_{GS} > -V_{th}$

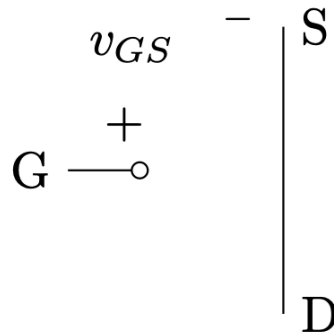

pMOS on: $v_{GS} < -V_{th}$

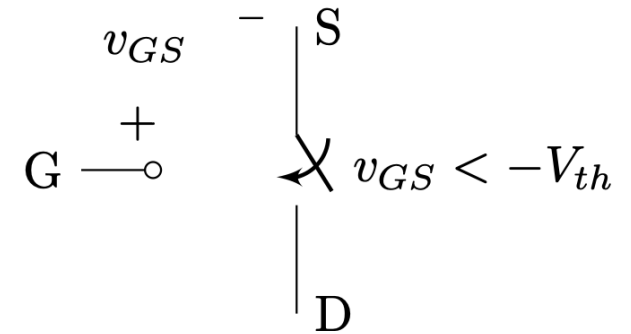

pMOS model

Information is stored on the computer in binary form

- An information variable represented by physical quantity
- For digital systems, the variable takes on discrete values
- Two level, or binary values are the most prevalent values in digital systems
- Binary values are represented by values or ranges of values of physical quantities

Binary logic Implemented with MOS



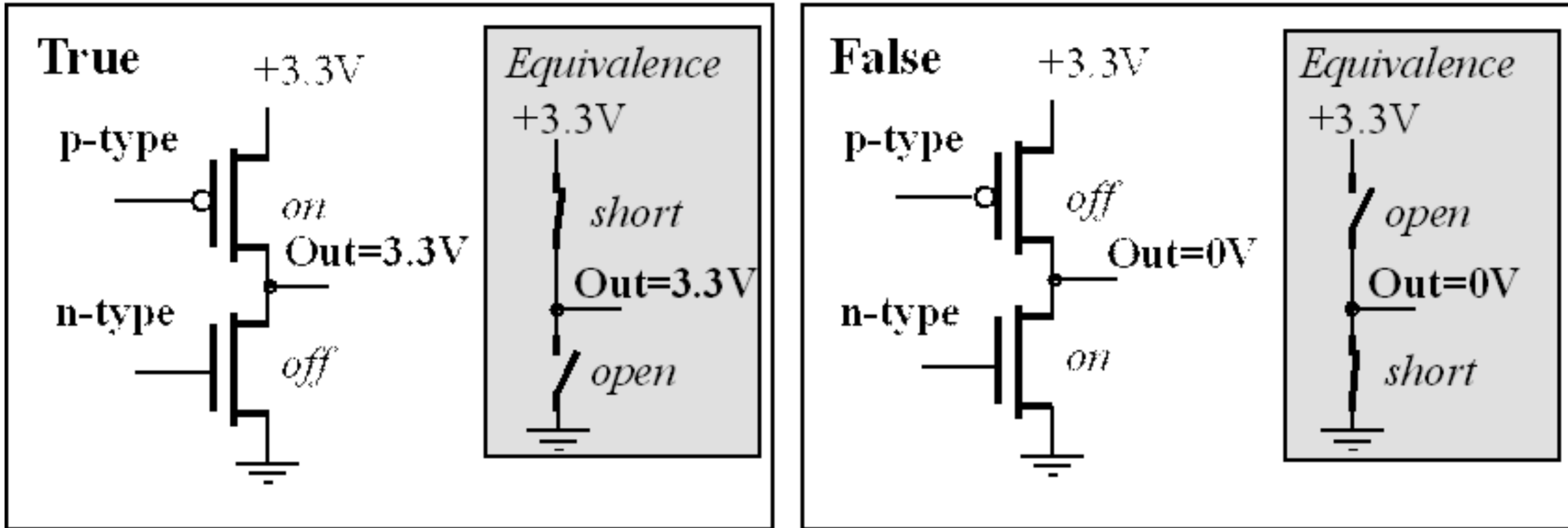


Figure 4.1. A binary bit is true if a voltage is present and false if the voltage is 0.

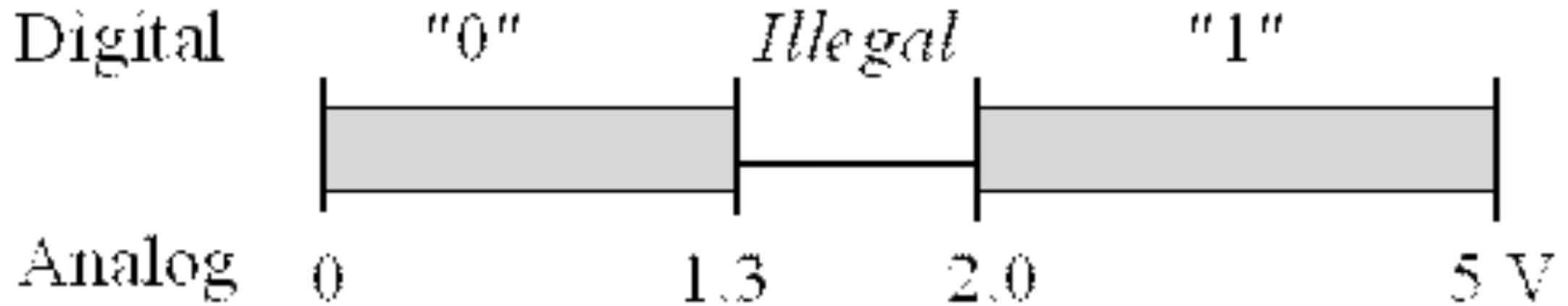Binary logics are represented by values or ranges of values of physical quantities




An implementation of 01100111

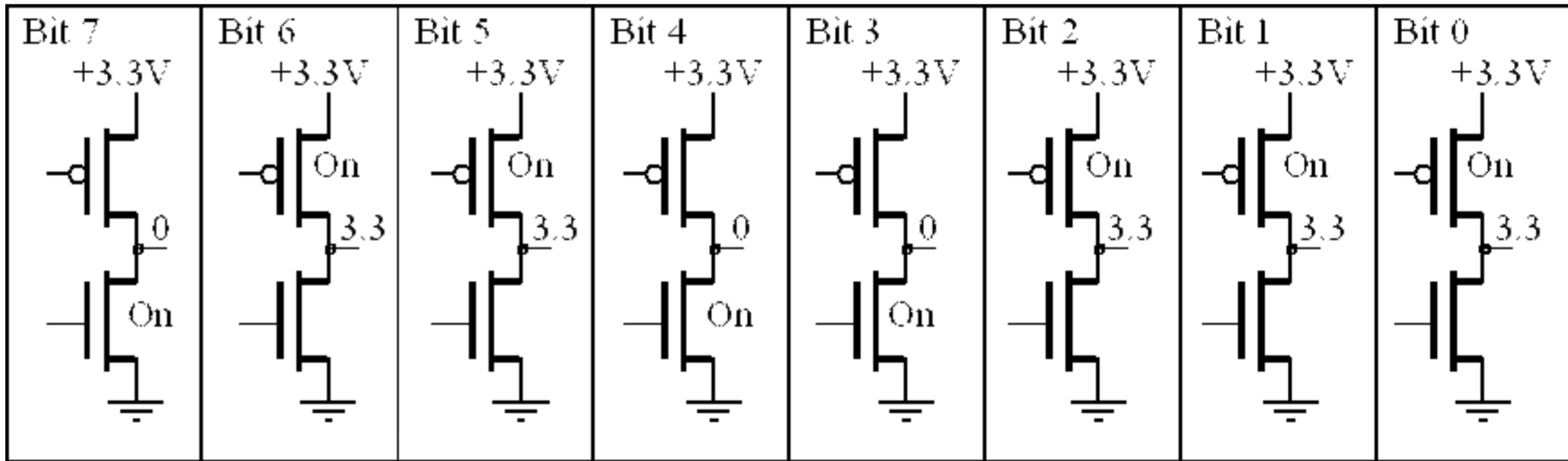

Digital logic of NOT gate

Digital logic

Buffer

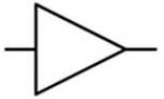


Input	Output
0	0
1	1

AND



A	B	Output
0	0	0
1	0	0
0	1	0
1	1	1

OR

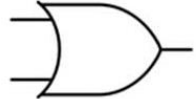


A	B	Output
0	0	0
1	0	1
0	1	1
1	1	1

XOR




A	B	Output
0	0	0
1	0	1
0	1	1
1	1	0

NOT gate

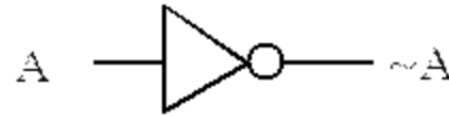


A	$\sim A$
0	1
1	0

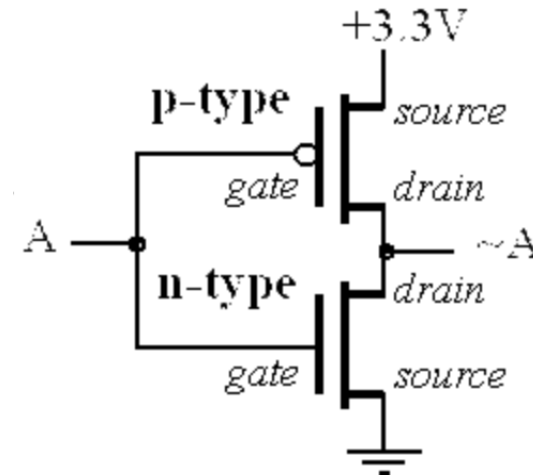


A	p-type	n-type	$\sim A$
0 V	active	off	+3.3V
+3.3V	off	active	0V

Practice

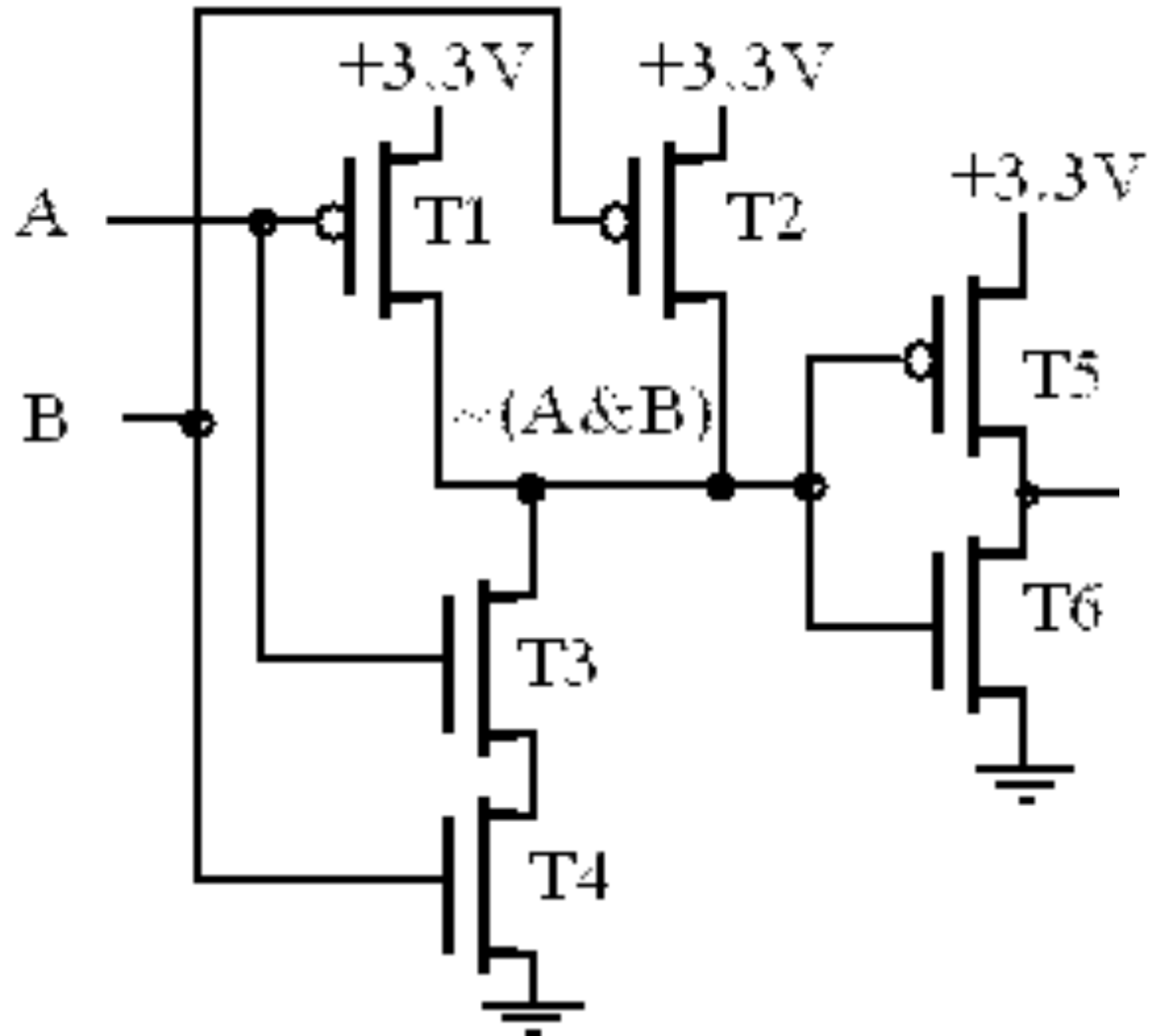

Practice

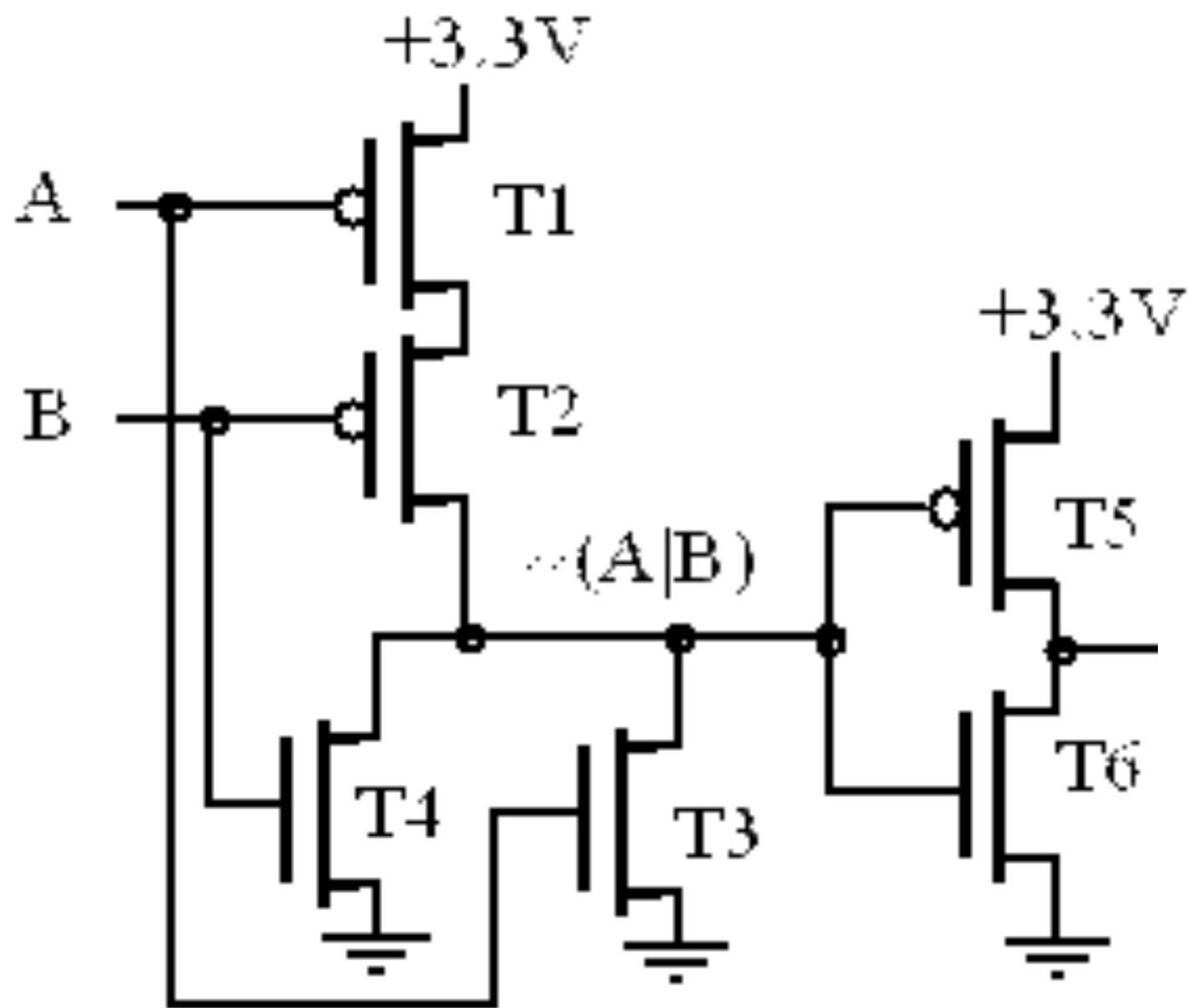

Digital logics by bit or Boolean

$$\begin{array}{rcl} A & = & 01100111 \\ B & = & \underline{11110000} \\ A \& B & & 01100000 \end{array}$$

$$\begin{array}{rcl} A & = & 01100111 \\ B & = & \underline{11110000} \\ A | B & & 11110111 \end{array}$$

$$\begin{array}{rcl} A & = & 01100111 \\ B & = & \underline{11110000} \\ A \&\& B & & 1 \end{array}$$

$$\begin{array}{rcl} A & = & 01100111 \\ B & = & \underline{11110000} \\ A | | B & & 1 \end{array}$$

Boolean Algebra

$A \& B = B \& A$	Commutative Law
$A \mid B = B \mid A$	Commutative Law
$(A \& B) \& C = A \& (B \& C)$	Associative Law
$(A \mid B) \mid C = A \mid (B \mid C)$	Associative Law
$(A \mid B) \& C = (A \& C) \mid (B \& C)$	Distributive Law
$(A \& B) \mid C = (A \mid C) \& (B \mid C)$	Distributive Law
$A \& 0 = 0$	Identity of 0
$A \mid 0 = A$	Identity of 0
$A \& 1 = A$	Identity of 1
$A \mid 1 = 1$	Identity of 1
$A \mid A = A$	Property of OR
$A \mid (\sim A) = 1$	Property of OR
$A \& A = A$	Property of AND
$A \& (\sim A) = 0$	Property of AND
$\sim(\sim A) = A$	Inverse
$\sim(A \mid B) = (\sim A) \& (\sim B)$	De Morgan's Theorem
$\sim(A \& B) = (\sim A) \mid (\sim B)$	De Morgan's Theorem

Practice


A	B	C	A & (B C)
$0100_2 = 4$	$0101_2 = 5$	$0110_2 = 6$	
$0111_2 = 7$	$1010_2 = 10$	$0001_2 = 1$	
$1110_2 = 14$	$1001_2 = 9$	$0111_2 = 7$	

Practice

A	B	C	A && (B C)
True	False	False	
True	False	True	
False	True	False	
True	True	False	

Digital logic for storing a bit

Set-Reset Latch

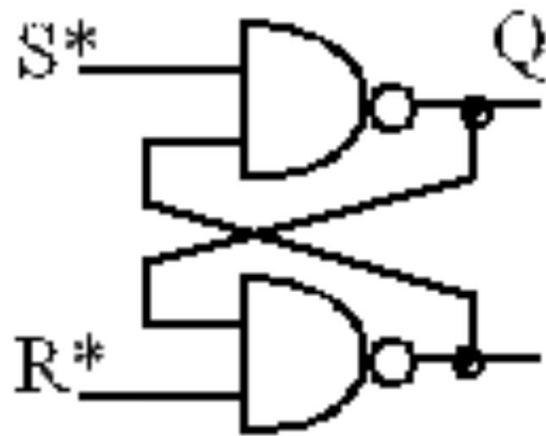


Truth Table		
Input		Output
Set	Reset	Q
Low	Low	Last State
Low	High	Low
High	Low	High
High	High	Unpredictable


Digital logic for storing a bit

Two inputs: D (data) and WE (write enable)

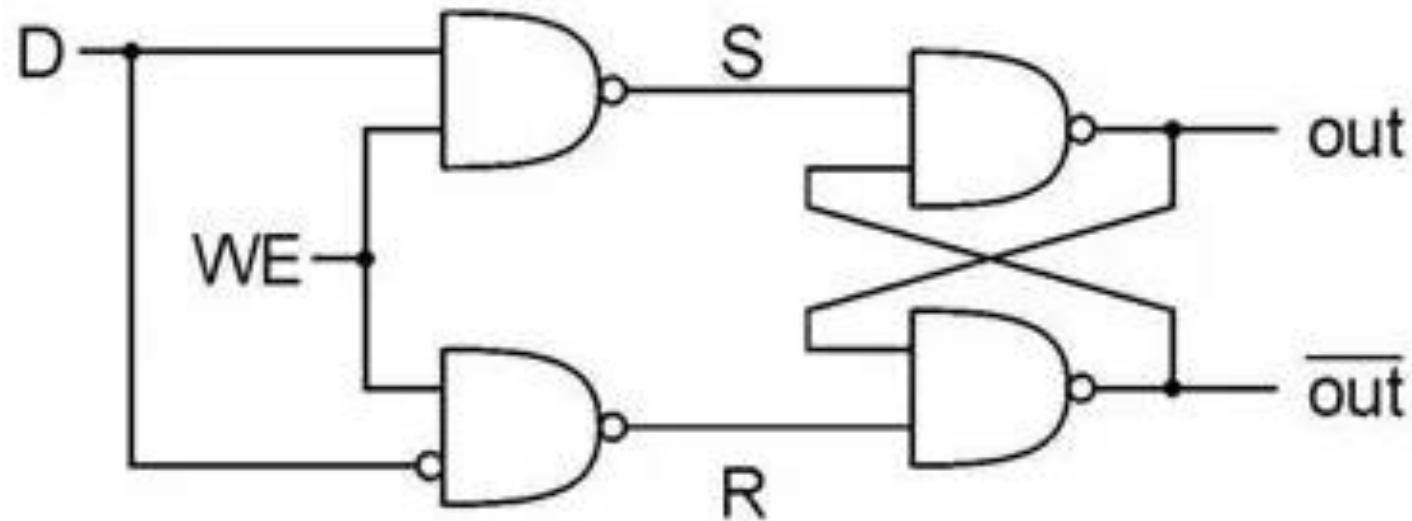
- when **WE = 1**, latch is set to **value of D**
 - $S = \text{NOT}(D)$, $R = D$
- when **WE = 0**, latch holds **previous value**
 - $S = R = 1$





Digital information stored in memory

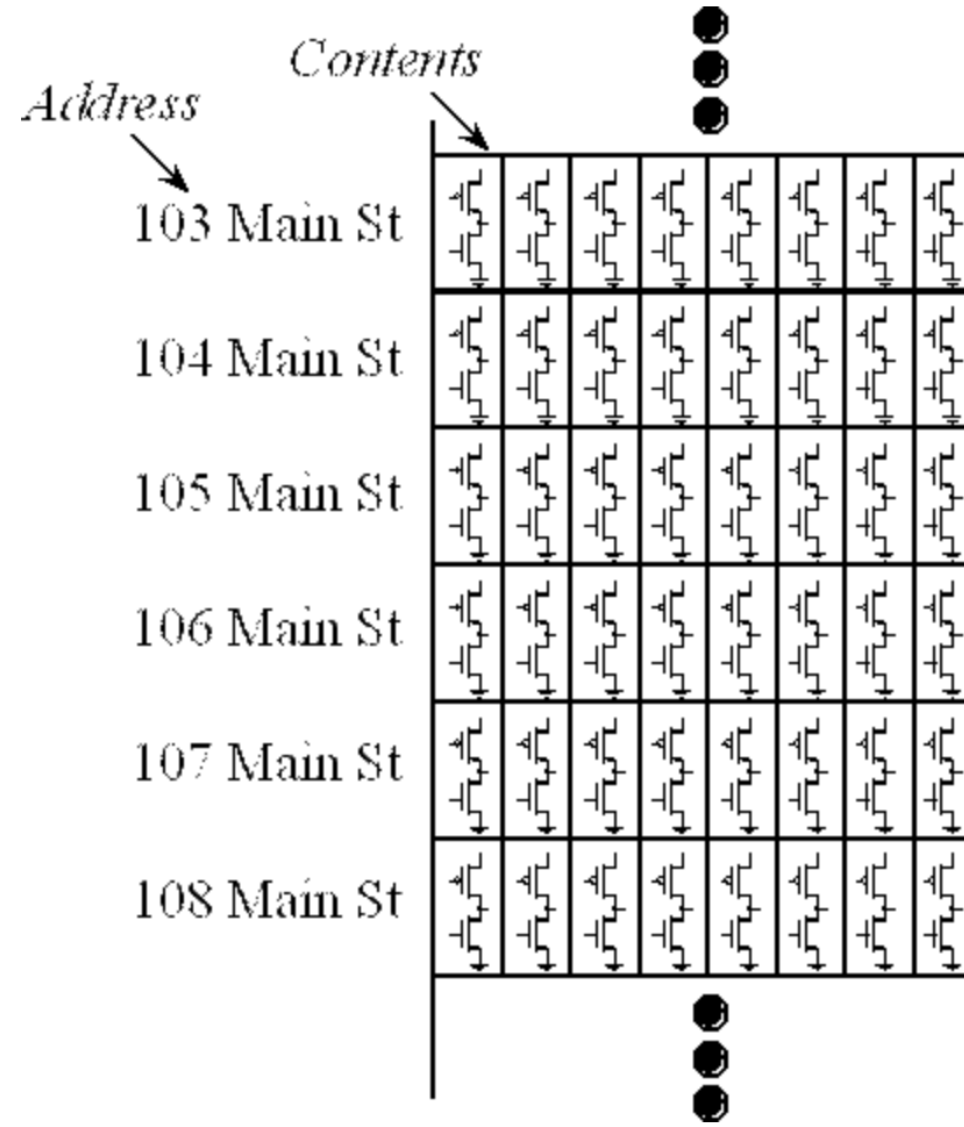

Binary adder

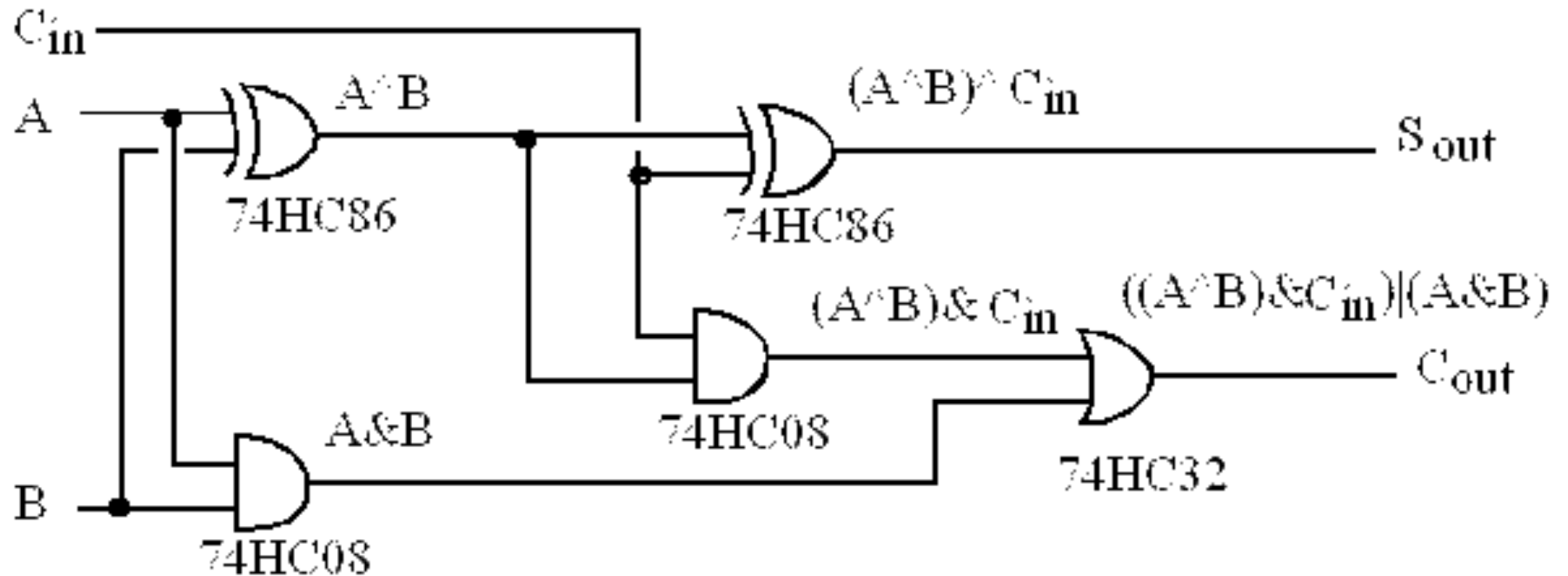

8-bit adder

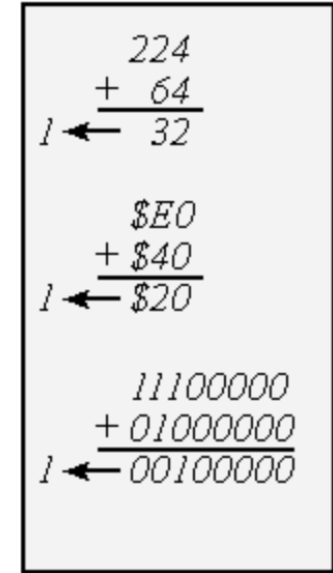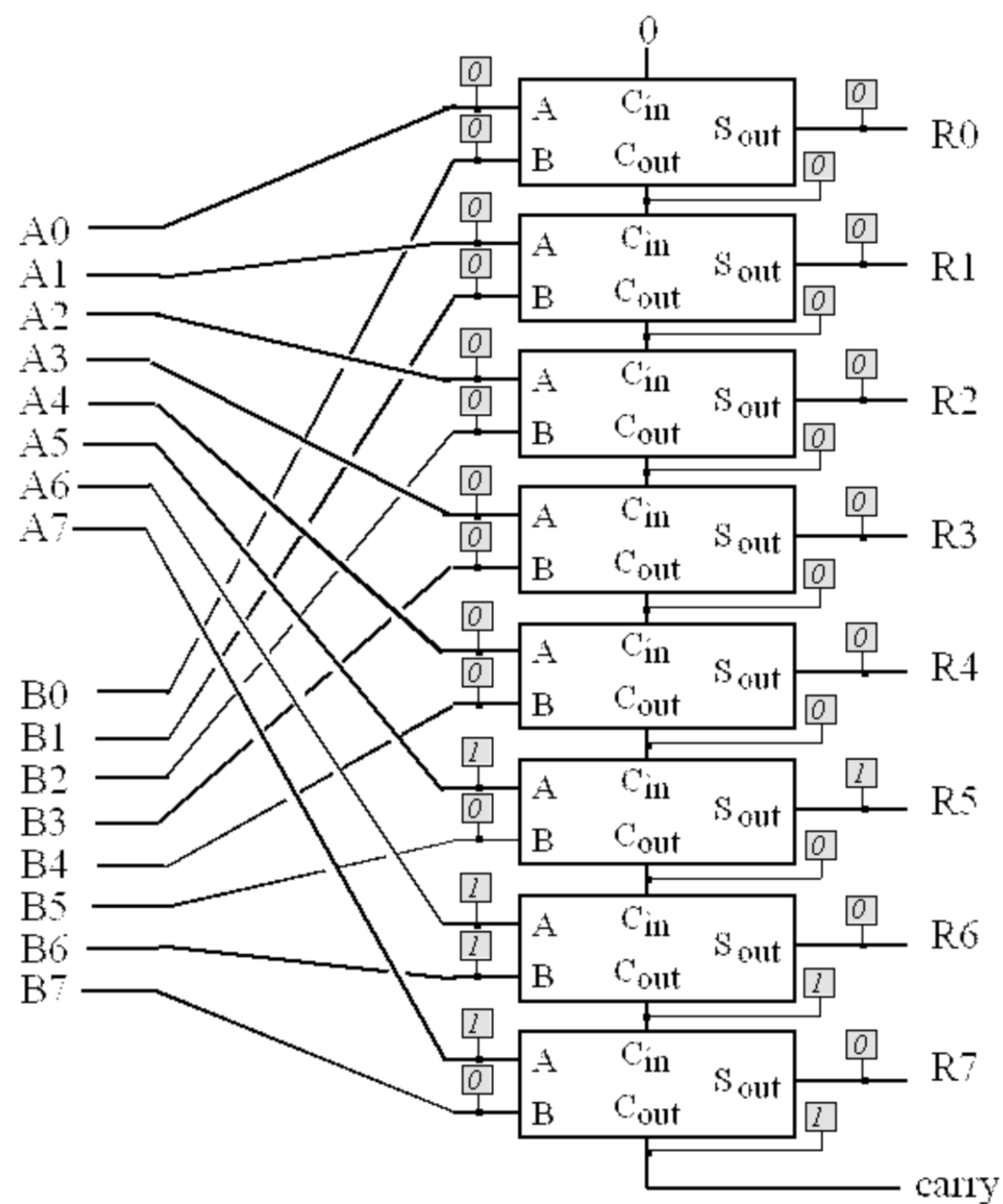

Common abbreviations for large numbers

<i>Value</i>	<i>SI Decimal</i>	<i>SI Decimal</i>
1000^1	k	kilo-
1000^2	M	mega-
1000^3	G	giga-
1000^4	T	tera-
1000^5	P	peta-
1000^6	E	exa-
1000^7	Z	zetta-
1000^8	Y	yotta-

<i>Value</i>	<i>IEC Binary</i>	<i>IEC Binary</i>
1024^1	Ki	kibi-
1024^2	Mi	mebi-
1024^3	Gi	gibi-
1024^4	Ti	tebi-
1024^5	Pi	pebi-
1024^6	Ei	exbi-
1024^7	Zi	zebi-
1024^8	Yi	yobi-

Recap: Running LEDs with digital logics


- <https://wokwi.com/projects/447390165530456065>

Virtual lab session: Binary adder for LED1 and LED2

- Can you implement a binary adder for LED1 and LED2?

Virtual lab session: Binary adder for LED1 and LED2

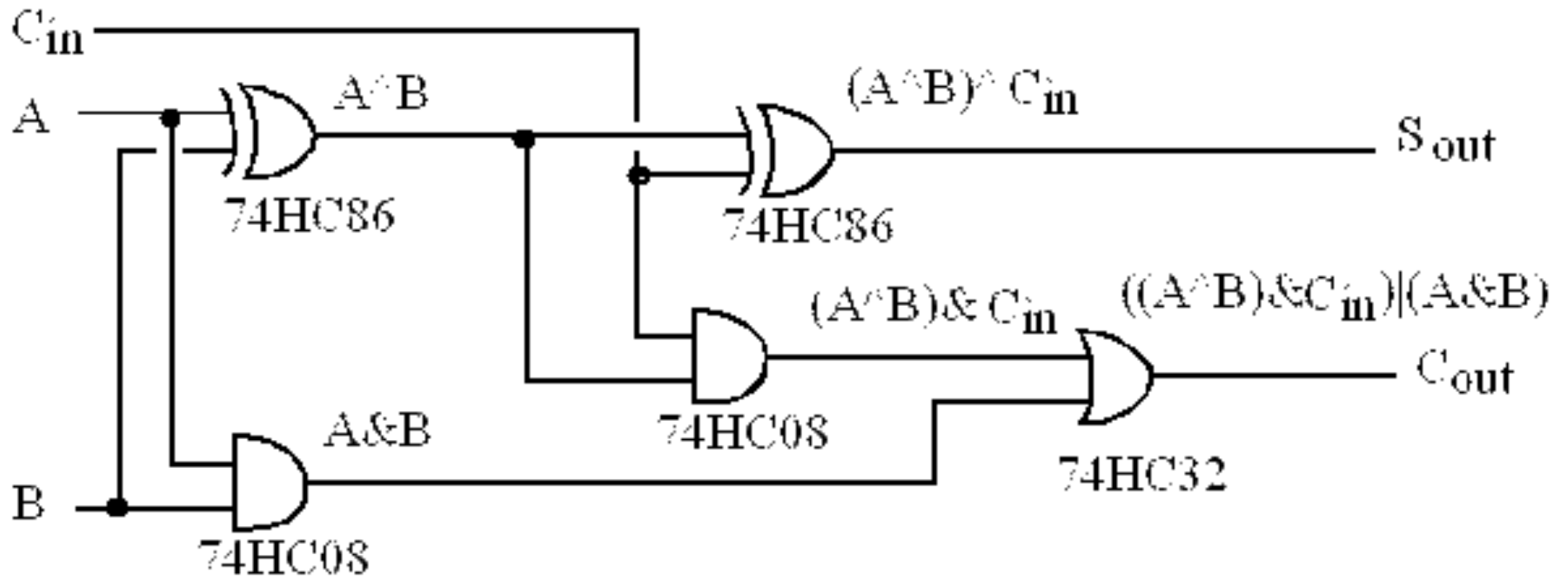- Can you implement a binary adder for LED1, LED2 and LED3 (carry) ?



Thank you!